

Name: Ritah Tastia Abedin Course Code: EEE 6141

ID: 1922180042 Sec-08 Faculty: SSHI



Chapters 5 & 6 Exercise - 5.6 → 22, 23, 25, 38

~~5.7 → 24, 38, 39~~


~~25, 38~~

5.6

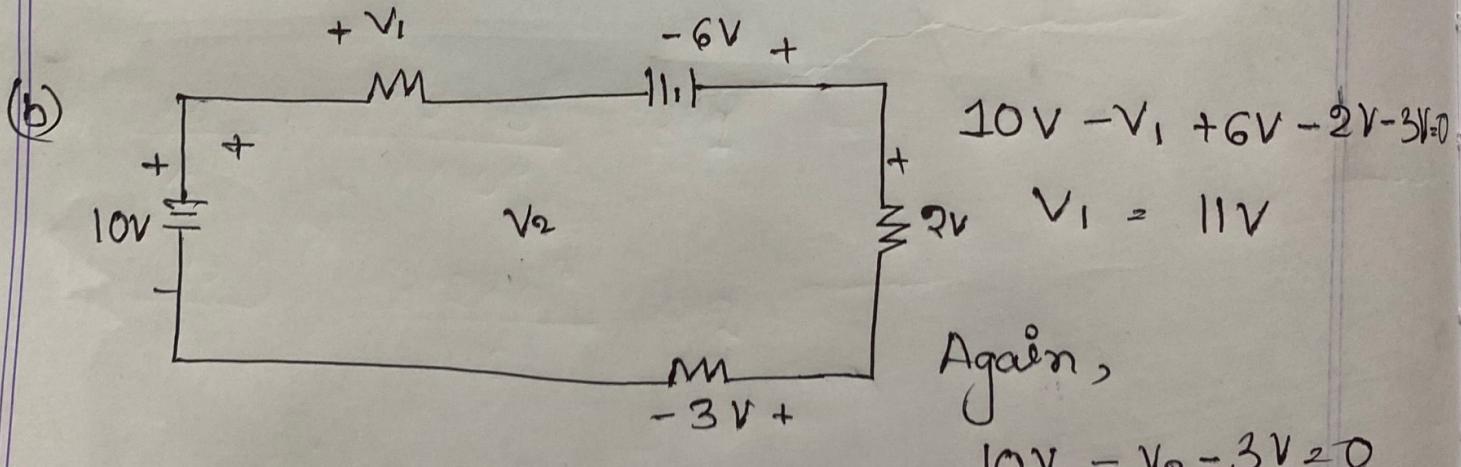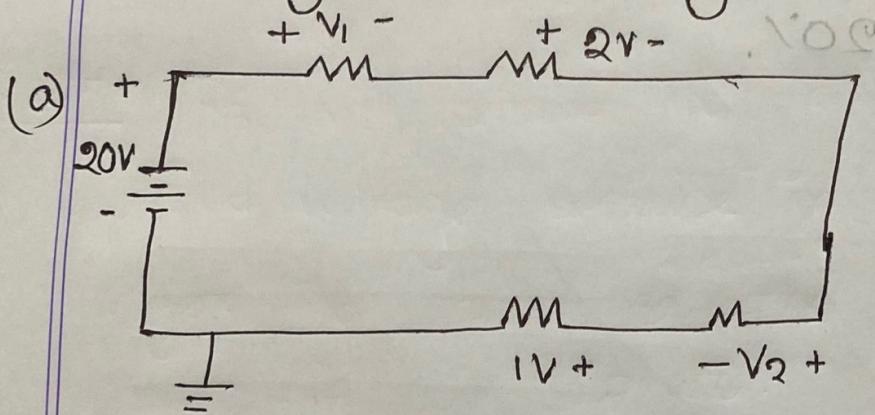23. Using KVL, finding the unknown voltage.




22.

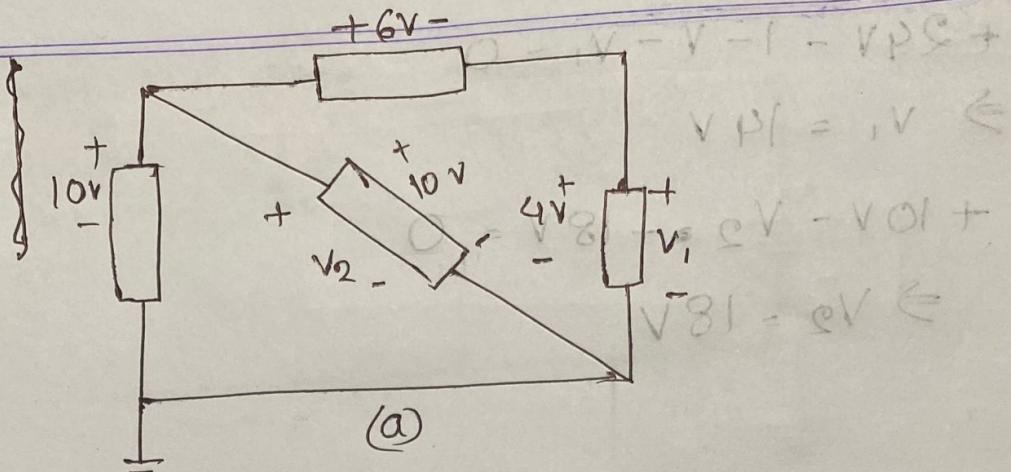

P.A

$$+10V - V_2 = 0$$

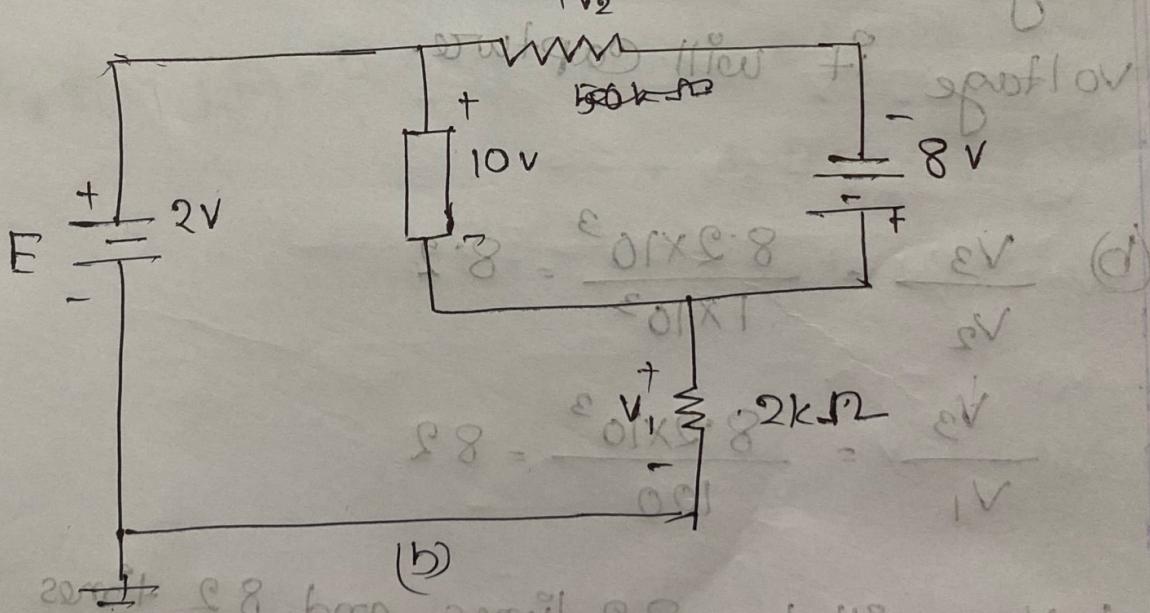eff $V_2 = 10V$ from the given circuit
eff $+10V - 6V - V_1 = 0$ becomes open bridge
bridge eff $V_1 = 4V$ from the given circuit




open circuit $20k\Omega$ $\frac{2}{8} = \frac{1}{4}$ $20k\Omega$ $\frac{1}{4} = 5k\Omega$
from the given circuit $8V$ is the output voltage

$$+24V - 1 - V - V_1 = 0$$

$$\Rightarrow V_1 = 14V$$

$$+10V - V_2 - 18V = 0$$

$$\Rightarrow V_2 = 18V$$

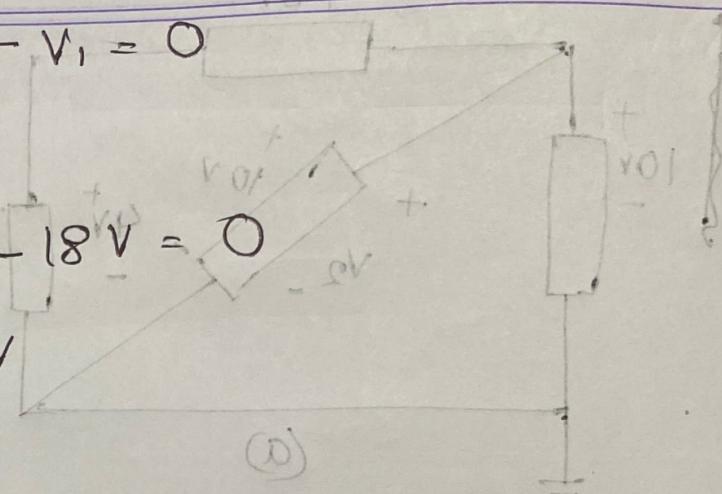

5.7


$$0 - 5V - 10V +$$

25(a) R_3 will receive the largest share of the applied voltage because in a series circuit the larger the resistance, the more of the applied voltage it will capture.

$$(b) \frac{V_3}{V_2} = \frac{8.2 \times 10^3}{1 \times 10^3} = 8.2$$

$$\frac{V_3}{V_1} = \frac{8.2 \times 10^3}{100} = 82$$

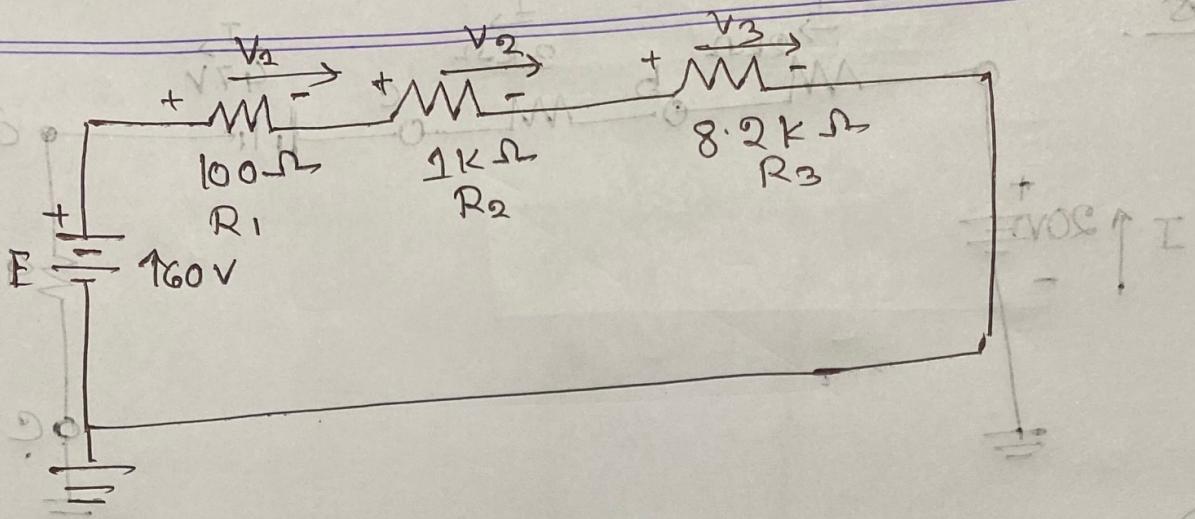$\therefore V_3$ will be 8.2 times and 82 times larger compared to V_2 and V_1 , respectively



$$A_{mE} = \frac{V_{OC} - V_{FP}}{R_{LP} + R_{KE} + R_{KC}} = I \quad (1)$$

$$\begin{aligned}
 (2) \quad V_{R_3} &= R_3 \frac{E}{R_T} = R_{KC} \times A_{mE} = 15V \\
 &= 8.2 \times 10^3 \frac{60}{9.3 \times 10^3} \times A_{mE} = 52.9V \\
 &= 52.9V = R_{KC} \times A_{mE} = 52.9V
 \end{aligned}$$


$$\begin{aligned}
 (3) \quad V_{R_2, R_3} &= (R_2 + R_3) \cdot \frac{E}{R_T} = (4 + 8.2) \times 10^3 \cdot \frac{60}{9.3 \times 10^3} \\
 &\approx 5.24 \times 10^3 = 59.4V
 \end{aligned}$$

$$V_{BE} = V_C + V_B + V_{OC} = 0V$$

$$\Delta V = 5.24 - 59.4V$$

$$\Delta V = 0V$$

38.

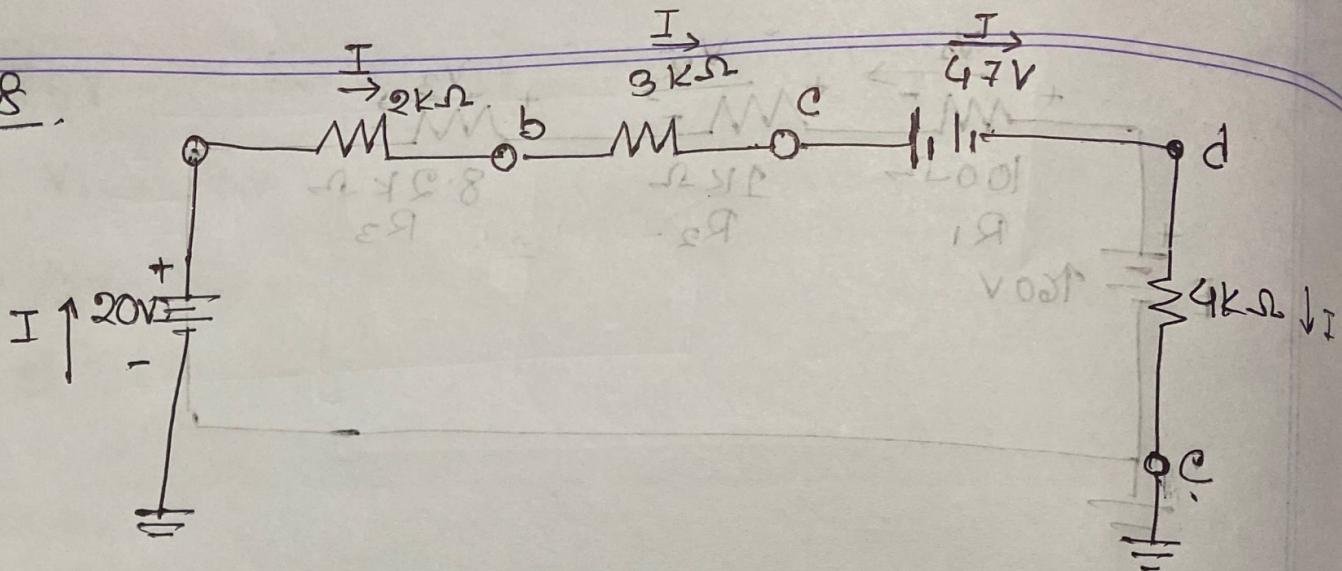

$$\text{a) } I = \frac{47V - 20V}{2k\Omega + 3k\Omega + 4k\Omega} = 3mA$$

$$V_{R1} = 3mA \times 2k\Omega = 6V$$

$$V_{R2} = 3mA \times 3k\Omega = 9V$$

$$V_{R3} = 3mA \times 4k\Omega = 12V$$

$$V_a = 20V - \frac{1}{2} \cdot (R_2 + R_3) = 20V - \frac{1}{2} \cdot (3k\Omega + 4k\Omega) = 15V$$

$$V_b = 20V + 6V = 26$$


$$V_c = 20V + 6V + 9V = 35V$$

$$V_d = -12$$

$$V_e = 0V$$

Chapter - 6

24.

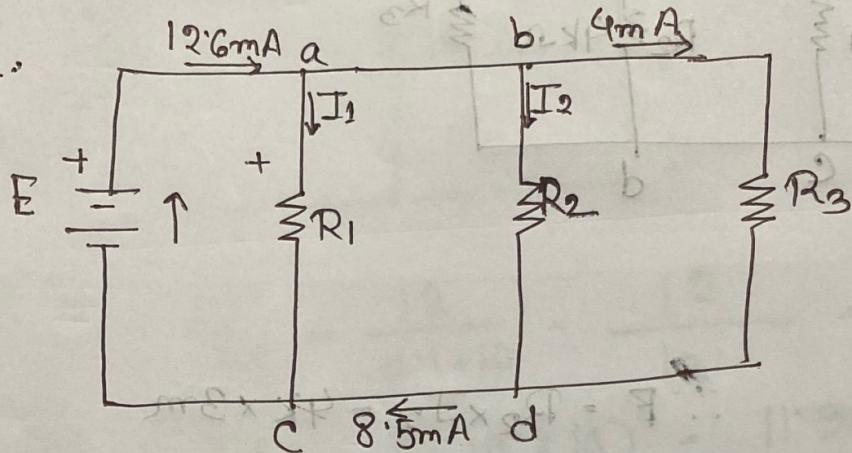

At a,

$$12.6 = I_1 + I_2 + 4 \text{mA}$$

$$I_1 + I_2 = 8.6 \text{mA}$$

$$\therefore I_1 = 8.6 - 4.5$$

$$= 4.1 \text{mA}$$

$$R_{1,2} = \frac{E}{I_1} = \frac{15}{4.1} = \frac{E}{I_1} = 3.68 \Omega$$


At d,

$$I_2 + 4 = \frac{8.5}{R_2} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_2 = 4.5 \text{mA}$$

$$R_{2,3} = \frac{E}{I_2} = \frac{15}{4.5} = \frac{E}{I_2} = 3.33 \Omega$$

$$R_2 = 7.5 \Omega$$

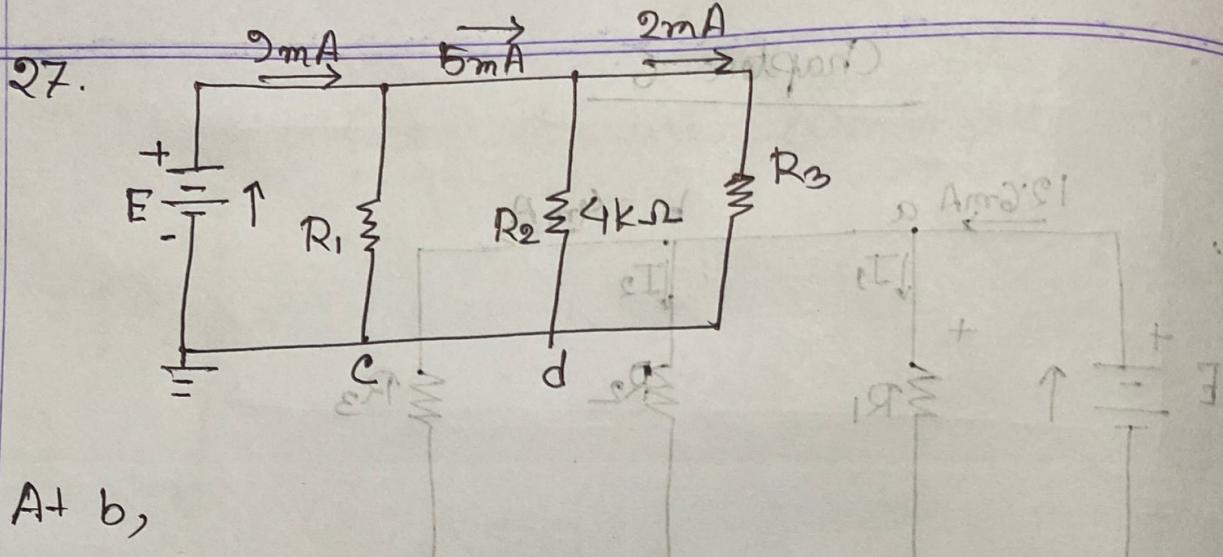

A + b,

$$5 = I_2 + 2$$

$$I_2 = 3 \text{ mA}$$

$$\therefore E = R_2 \times I_2 = 4k \times 3m \\ = 12 \text{ Volts}$$

At a,

$$9 = I_1 + 5$$

$$I_1 = 4 \text{ mA}$$


$$R_B = \frac{E}{2m} = \frac{12}{2m} = 6k\Omega$$

$$\therefore R_1 = \frac{E}{I_1} = \frac{12}{4m} = 3k\Omega$$

$$\therefore \frac{1}{R_T} = \frac{1}{3k} + \frac{1}{4k} + \frac{1}{6k} = P + \bar{c}I$$

$$R_T = 1.33k\Omega$$

38.

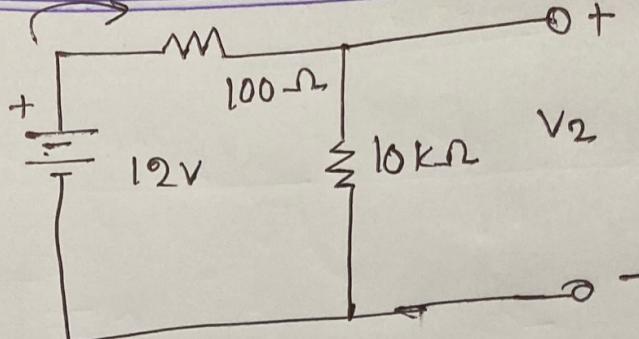


(a) $I_s = \frac{E}{R_T} = \frac{12}{0.1 + 10} = \frac{12}{10.1} = 1.188 \text{ mA}$

$V_2 = I_s R_2 = (1.188 \times 10) = 11.90 \text{ V}$

(b) $I = \frac{12 \text{ V}}{100} = 120 \text{ mA}$

(c) $V_2 = E = 12 \text{ V}$

39/

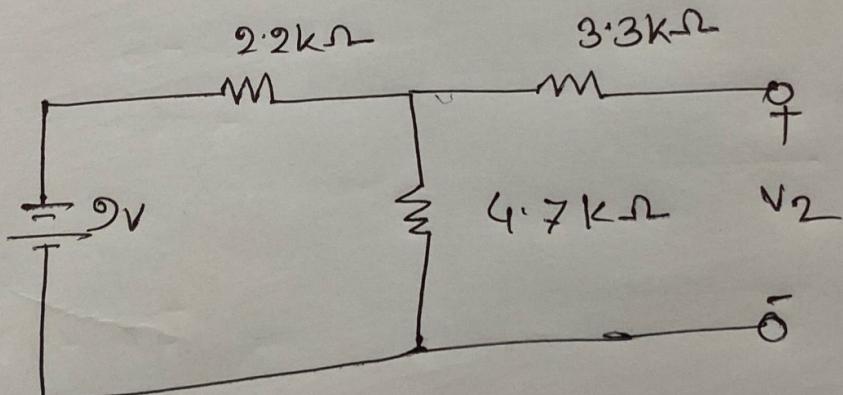

$V_2 = \frac{4.7 \times 9}{4.7 + 2.2} = \frac{42.3}{6.9} = 0.61$

(b) $V_2 = E = 9 \text{ V}$

(c) $V_2 = E = 9 \text{ V}$