



NORTH SOUTH UNIVERSITY
DEPARTMENT OF ELECTRICAL &
COMPUTER ENGINEERING

Assignment-2


Spring 2022

EEE141: Electrical Circuits I
Section: 08

Name: Rifah Tasfia Abedin
ID:1922180042

Section 6'3

16. Here,

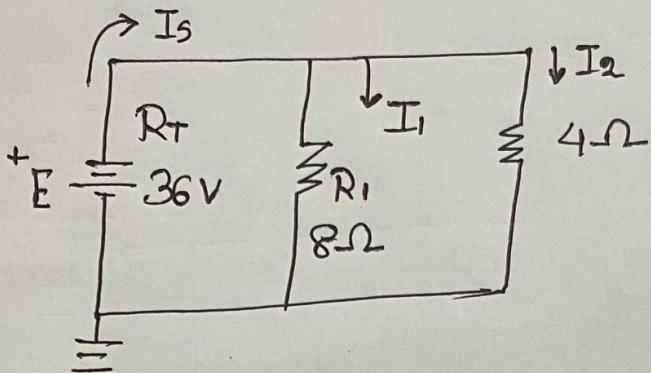

(a) From Circuit,

$$\begin{aligned}
 R_T &= R_1 \parallel R_2 \\
 &= 8\Omega \parallel 24\Omega \\
 &= \frac{8\Omega \times 24\Omega}{8\Omega + 24\Omega} \\
 &= 6\Omega
 \end{aligned}$$

(b) Here, the voltage source and the resistance are in parallel,

Therefore, $V_{R_1} = 36V$

$$V_{R_2} = 36V$$


(c) From Circuit,

$$I_S = \frac{E}{R_T} = \frac{36V}{6\Omega} = 6A$$

\therefore the source current is $I_s = 6A$

The current through the first branch,
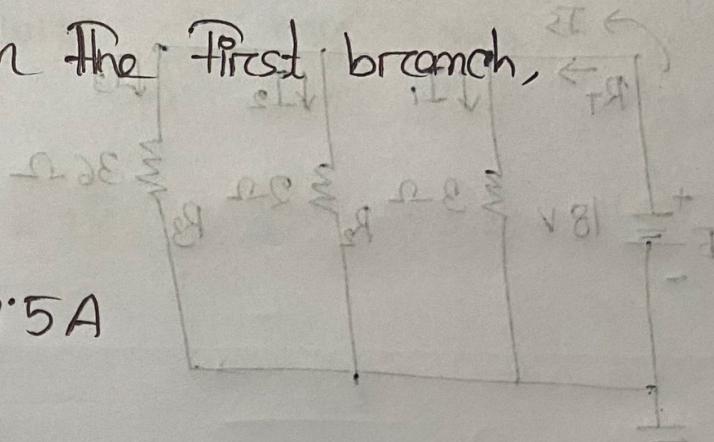
$$I_{R_1} = \frac{V}{R_1} = \frac{36V}{8\Omega} = 4.5A$$



The current through the second branch

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{36^2}{29\Omega} = 1.5 A$$


(b) By applying Kirchoff's current law,

$$I_S = I_{R_1} + I_{R_2}$$

$$\Rightarrow 6A = 4.5A + 1.5A$$

$$\Rightarrow 6A = 6A \quad \text{(checks)}$$

ii. Here,

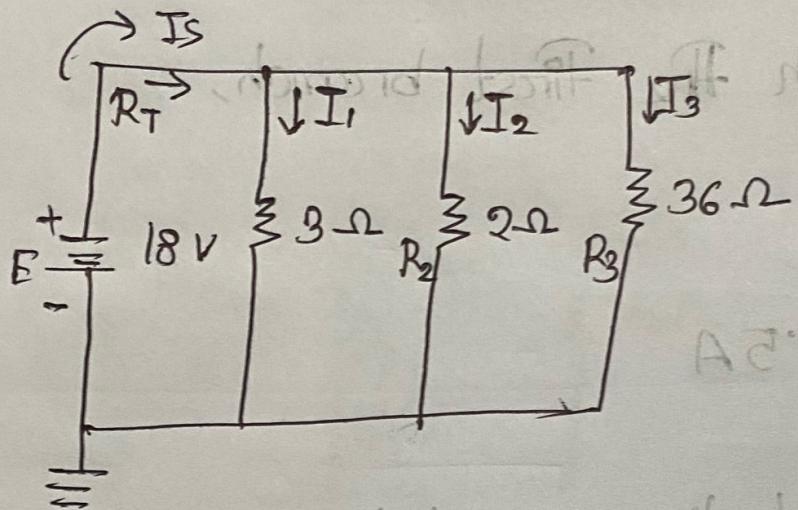

$$A.C.P. = \frac{V_{R_3}}{R_3} =$$

$$\frac{18V}{36\Omega} = 0.5A$$

(a) From Circuit,

$$R_T = \frac{\frac{1}{A.C.P.} - \frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$
$$= \frac{1}{0.3335 + 0.1115 + 0.0285}$$
$$= \frac{1}{472 \times 10^{-3}} \text{ A.C.P.} = A.C.P. \leftarrow$$
$$= 2.12\Omega$$

(b) Here,

Here, the voltage source the resistance to parallel.


Therefore,

$$V_{R_1} = V_{R_2} = V_{R_3} = 18V$$

(i) $I_S = \frac{E}{R_T}$

$$= \frac{18V}{2.12\Omega}$$

$$= 8.5A$$

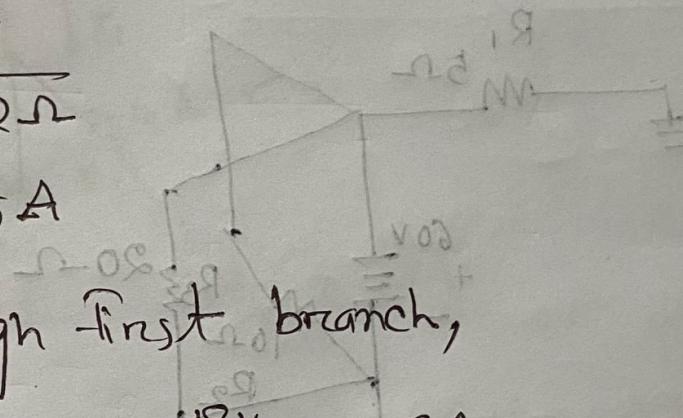

Current through first branch,

$$\therefore I_1 = \frac{V_{R_1}}{R_1} = \frac{18V}{3\Omega} = 6A$$

Current through second branch

$$I_2 = \frac{V_{R_2}}{R_2} = \frac{18V}{9\Omega} = 2A$$

Current through third branch

$$I_3 = \frac{V_{R_3}}{R_3} = \frac{18V}{36\Omega} = 0.5A$$

$$(20.0 + 21.0 + 28.0)$$


$$= 70.0$$

$$(d) I_s = I_1 + I_2 + I_3$$

$$\Rightarrow 8.5 A = (6A + 2A + 0.5A)$$

$$\Rightarrow 8.5 A = 8.5 A \text{ (checks)}$$

21.

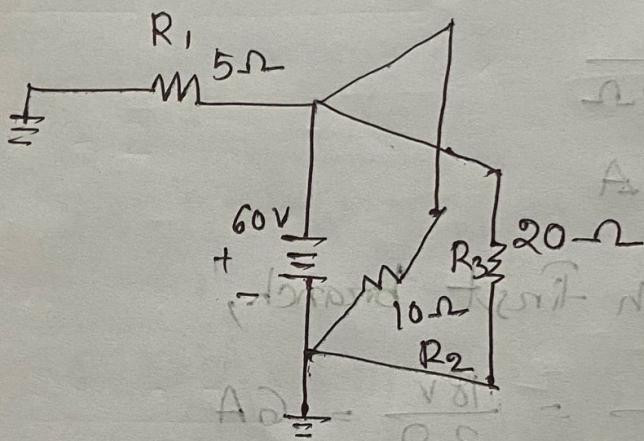

Total resistance, R_{total}

$$R_{\text{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{\text{total}} = \frac{1}{5\Omega} + \frac{1}{10\Omega} + \frac{1}{20\Omega}$$


$$= \frac{1}{0.25} + \frac{1}{0.15} + \frac{1}{0.05}$$

$$= 2.86 \Omega$$

\therefore The power delivered by the source $P = E \cdot I_S$

$$= E \cdot \frac{E}{R_T} = \frac{E^2}{R_T}$$
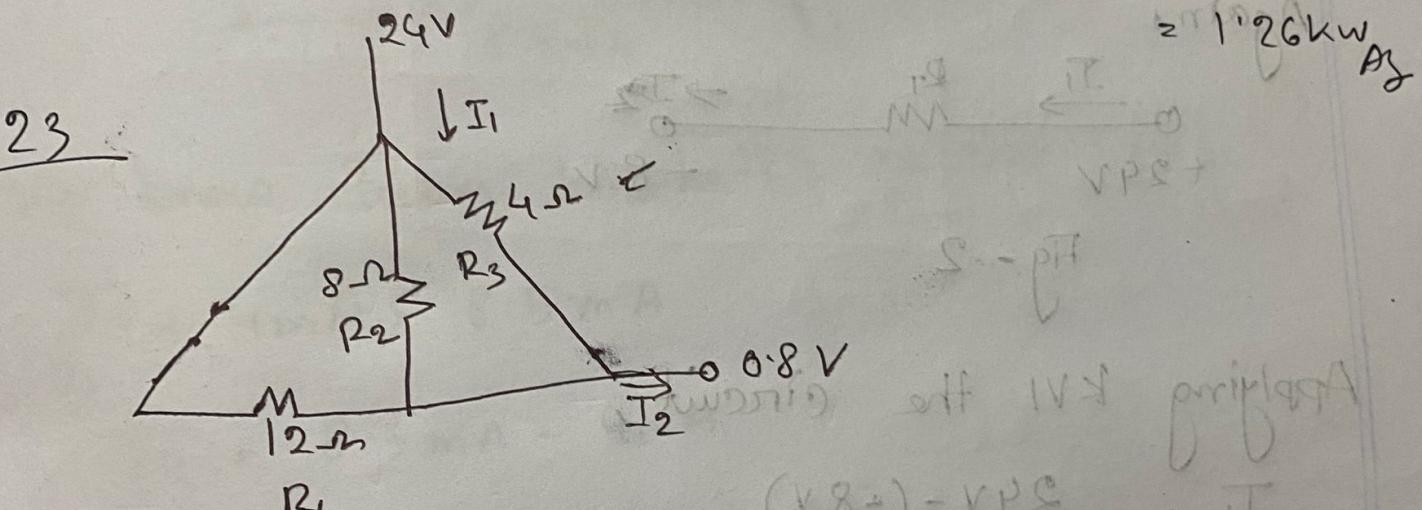
$$= \frac{(60V)(60V)}{2.86\Omega} = 1.26 \text{ kW}$$



(a) From circuit,

$$R_1 \parallel R_2$$

Considering $R_1 = 12\Omega$

$$R_2 = 8\Omega$$

$$R_3 = 4\Omega$$

$$R_T = \frac{R_{T_1} R_3}{R_{T_1} + R_3}$$

Here $R_T \parallel R_3$

$$= \frac{(4.8\Omega)(9\Omega)}{4.8\Omega + 4\Omega}$$

$$\frac{(V_{O2})(V_{O2})}{-8.8\Omega} = 2.182\Omega$$

Again,

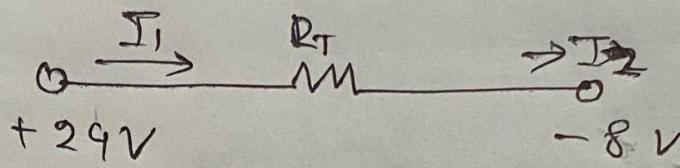


Fig - 2

Applying KVL the circuit,

$$I_1 = \frac{24V - (-8V)}{2.182\Omega}$$

$$= 14.67A$$

(b) Here, $P_L = \frac{V^2}{R} = \frac{(24V - (-8V))^2}{4\Omega}$

$$= 256V\cdot\Omega$$


(c) From Fig - 2, $I_2 = I_1$,

$$I_2 = 14.67A$$

Ans

6.5

24 Here,

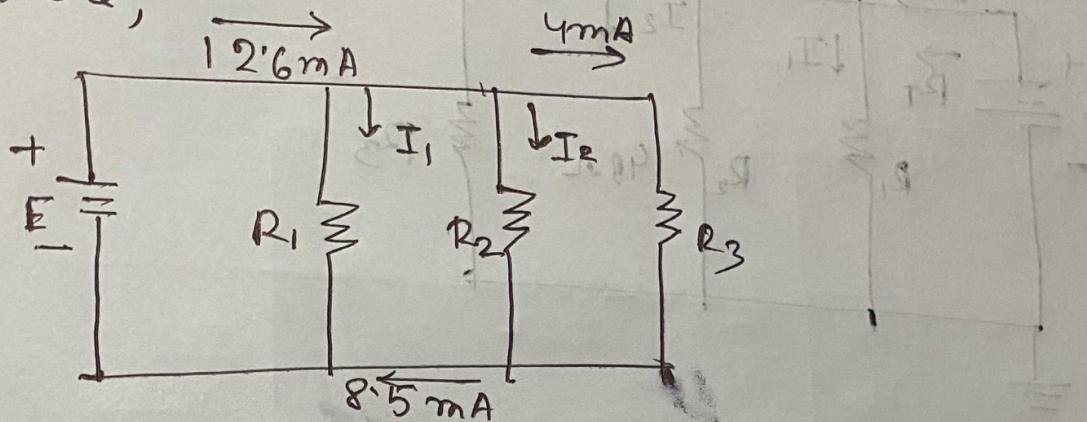

We know from Kirchhoff's Current Law,
 $I_1 + I_2 + I_3 = \text{AmS}$

$$I_2 + 4 \text{ mA} = 8.5 \text{ mA} \quad \text{AmS} = \text{AmS}$$

$$\Rightarrow I_2 = 8.5 \text{ mA} - 4 \text{ mA}$$

$$= 4.5 \text{ mA}$$


Again, $12.6 \text{ mA} = I_1 + I_2 + 4 \text{ mA}$

$$\Rightarrow 12.6 \text{ mA} = I_1 + 4.5 \text{ mA} + 4 \text{ mA}$$

$$\Rightarrow I_1 = 12.6 \text{ mA} - 8.5 \text{ mA}$$

$$= 4.1 \text{ mA}$$

27

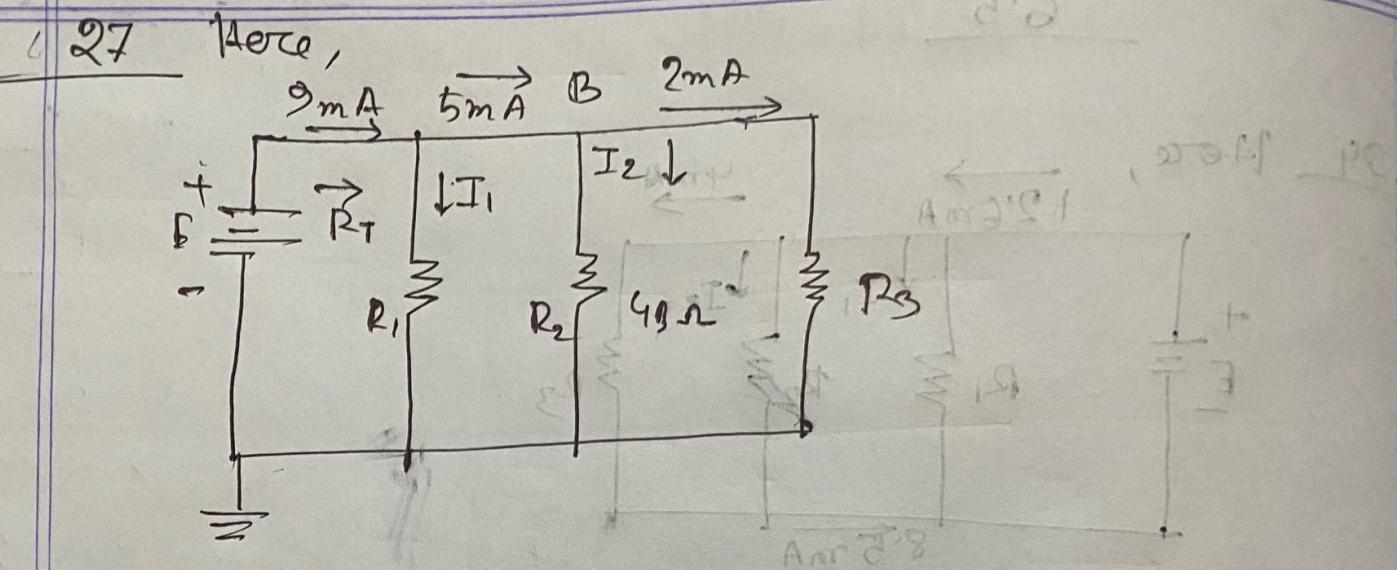

Applying Kirchhoff's law,

$$5\text{mA} = 2\text{mA} + I_2$$

$$\Rightarrow I_2 = 3\text{mA}$$

$$\text{So, } V_B = I_2 R_2$$

$$= (3\text{mA}) (9\Omega)$$

$$= 12\text{V}$$

Applying Kirchhoff current law at node A

$$9\text{mA} = 5\text{mA} + I_1$$

$$I_1 = 9\text{mA} - 5\text{mA}$$

$$= 4\text{mA}$$

So apply ohm's law,

$$E = I_1 R_1$$

$$R_1 = \frac{E}{I_1}$$

$$I_1 R_1 = \frac{12V}{2mA} = 3k\Omega$$

Apply Ohm's Law,

$$E = I_3 R_3$$

$$= \frac{E}{I_3}$$

$$A2 = \frac{12V}{2mA} = 6k\Omega$$

Again, $E = I_T R_T$

$$R_T = \frac{E}{I_T}$$

$$(A2) \frac{1}{\epsilon}$$

$$AC =$$

$$= \frac{12V}{2mA}$$


$$= 1.33k\Omega \text{ Ans}$$

$$AC = AC_{max}$$

29

Hence,

$$I_1 = 6A$$

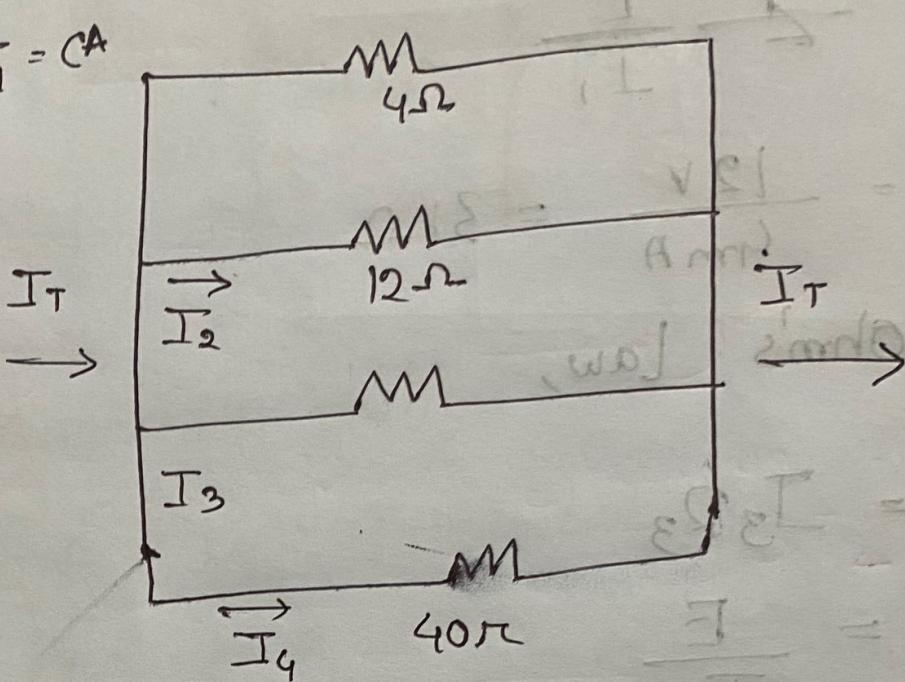

Since,

$$I_2 = \frac{4\Omega}{12\Omega} I_1$$

$$= \frac{1}{3} I_1$$

$$= \frac{1}{3}(6A)$$

$$= 2A$$

Here, $I_1 = 6A$
Ans

Again, $I_2 = \frac{4\Omega}{2\Omega} I_1$

$$= 2 I_1$$

$$= 2 \times 6A = 12A$$

$$\text{Again, } I_4 = \frac{4\Omega}{40\Omega} I_1$$

$$= \frac{1}{10} I_1$$

$$= \frac{1}{10} \times 6A$$

$$= 0.6A$$

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$= (6A + 2A + 12A + 0.6A)$$

$$= 20.6 A$$

Ans


$$(A_{m28}) \left(\frac{\Omega \times 3}{\Omega \times 3 + 5} \right) = A_{m8}$$

$$(A_{m28}) \left(\frac{\Omega \times 3}{\Omega \times 3 + 5} \right) = A_{m8}$$

$$(\Omega \times 3) \left(\frac{A_{m28}}{A_{m8}} \right) = \Omega \times 3 + 5$$

$$\Omega \times 3 - (\Omega \times 3) \left(\frac{A_{m28}}{A_{m8}} \right) = 5$$

33 Here,

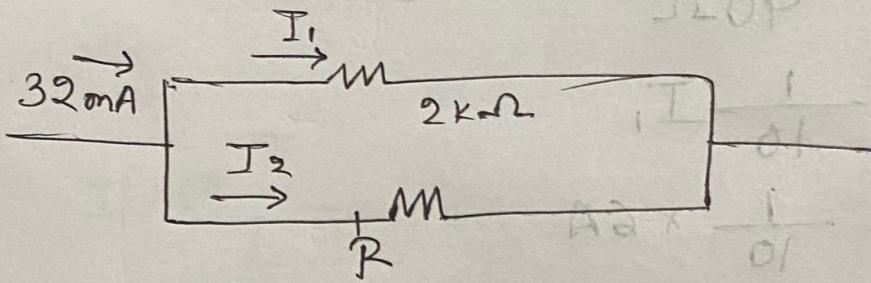

(Q) Apply Kirchoff's current,

$$I_1 + I_2 = 32 \text{ mA}$$

$$\Rightarrow 3I_2 + I_2 = 32 \text{ mA} \quad [\text{Relation in two branches}]$$

$$\Rightarrow 4I_2 = 32 \text{ mA} \quad I_1 = 3I_2$$

$$I_2 = 8 \text{ mA}$$

Using current divider rule,

$$I_2 = \left(\frac{2 \text{ k}\Omega}{R + 2 \text{ k}\Omega} \right) (32 \text{ mA})$$

$$\Rightarrow 8 \text{ mA} = \left(\frac{2 \text{ k}\Omega}{R + 2 \text{ k}\Omega} \right) (32 \text{ mA})$$

$$\Rightarrow R + 2 \text{ k}\Omega = \left(\frac{32 \text{ mA}}{8 \text{ mA}} \right) (2 \text{ k}\Omega)$$

$$\therefore R = (4)(2 \text{ k}\Omega) - 2 \text{ k}\Omega \\ = 6 \text{ k}\Omega$$


∴ Unknown Resistance R is $6 \text{ k}\Omega$

$$\begin{aligned}
 & (b) I_1 + I_2 = 32 \text{ mA} \\
 & \Rightarrow 3I_2 + I_2 = 32 \text{ mA} \quad \text{Now here, } I_1 = 3I_2 \\
 & \Rightarrow 4I_2 = 32 \text{ mA} \\
 & \therefore I_2 = 8 \text{ mA} \quad \frac{E}{R} = \epsilon - IR
 \end{aligned}$$

So,


$$\begin{aligned}
 I_1 &= 3I_2 \\
 &= 3(8 \text{ mA}) \\
 &= 24 \text{ mA}
 \end{aligned}$$

$\therefore I_1 = 24 \text{ mA}$

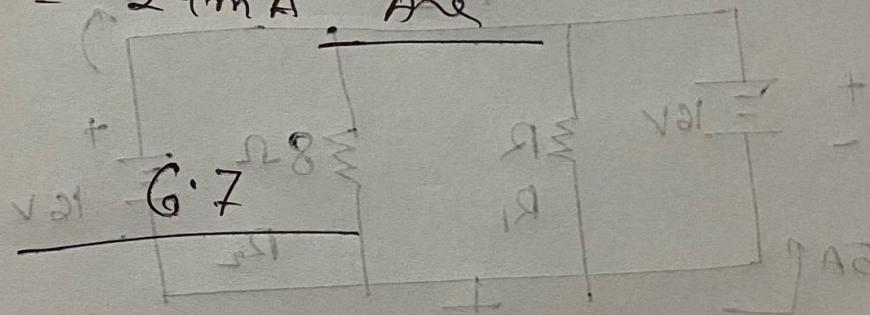

36

Here,

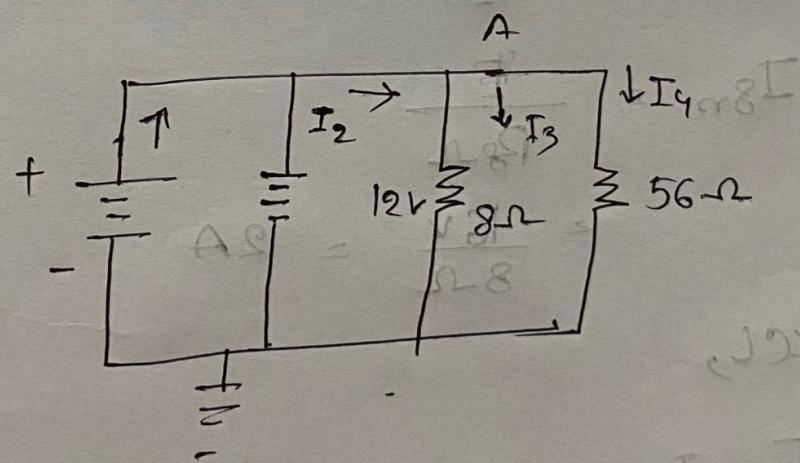

(a) Here

$$R_T = 8\Omega \parallel 56\Omega = 7\Omega$$

In parallel voltage circuit, the currents from the sources are same so,


$$I_2 = I_3 = \frac{E}{R_f}$$

$$= \frac{12V}{7\Omega} = 1.71A$$


$$AmP = sI$$

$$\text{Again, } I_1 = \frac{1}{2} I_2 = \frac{1}{2} (1.71A) = 0.86A$$

37 Here,

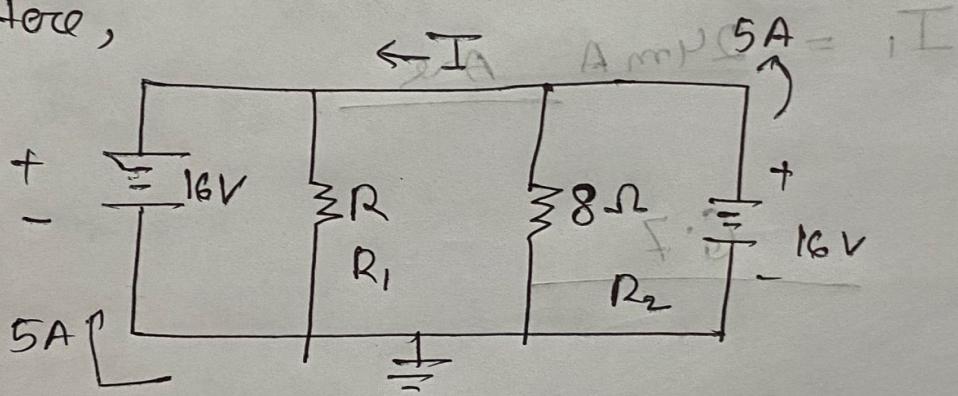

Here,

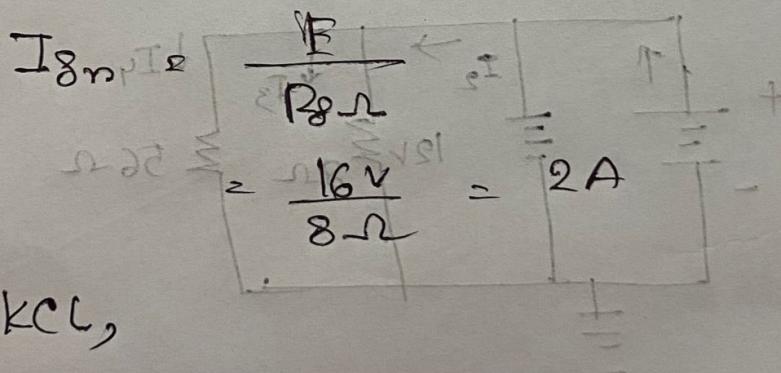

Using KCL,

$$I = I_3 = I_{g-n}$$

$$= 5A - 2A = 2A$$

$$= 3A$$


$$\therefore I_R = I + I_S$$

$$= 3A + 5A$$

$$= 8A$$

$$\therefore R = \frac{E}{I_R} = \frac{16V}{8A} = 2\Omega \text{ Ans.}$$

6.8

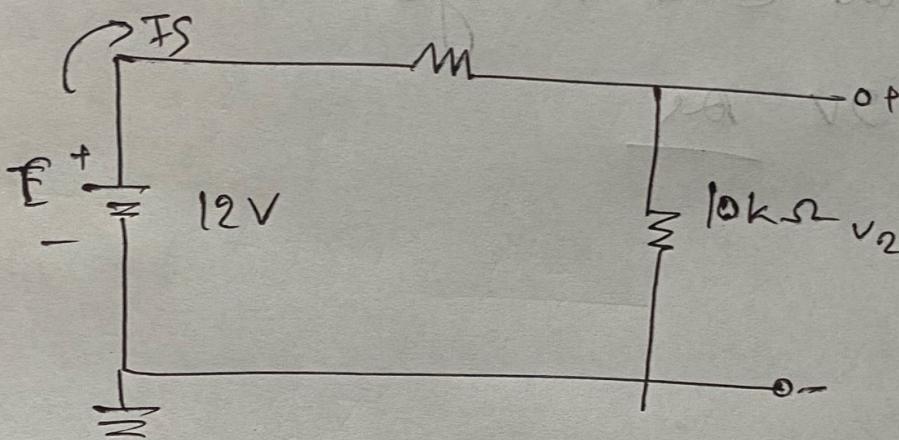

$$(a) I_S = \frac{E}{R_T} = \frac{E}{R_1 + R_2} =$$


$$I_S = \frac{12V}{100\Omega + 10000\Omega} = 1.188mA$$

$$\therefore V_L = (1.188mA)(10k\Omega)$$



$$= 11.92$$

$$(b) I_S = \frac{E}{R_1} = \frac{12V}{100\Omega} = 0.12A$$

(c)

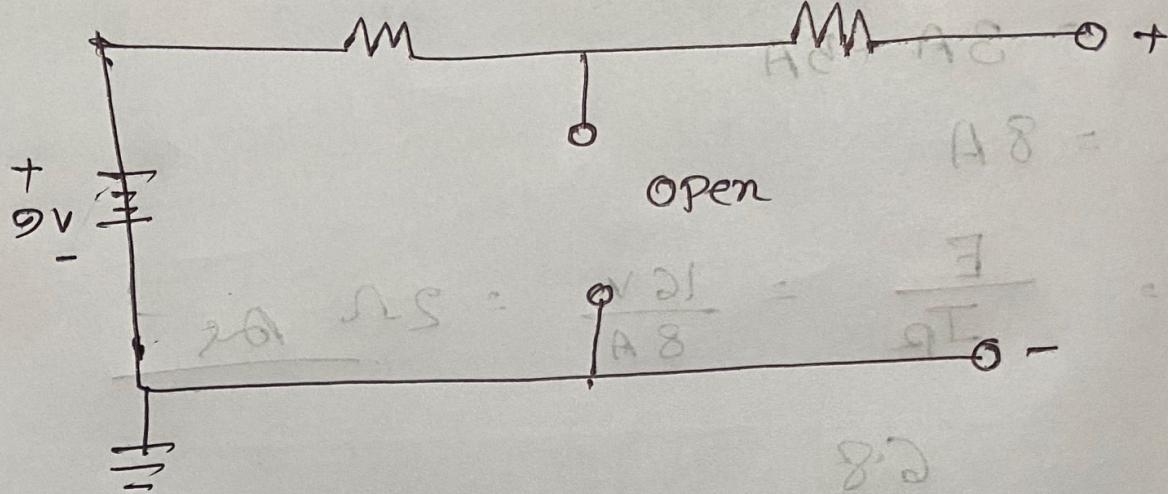

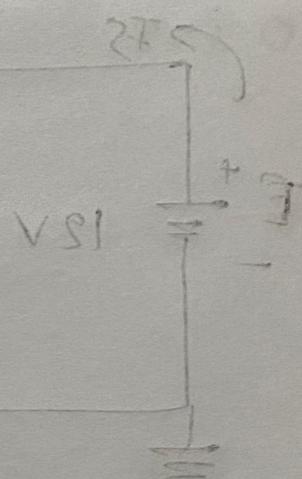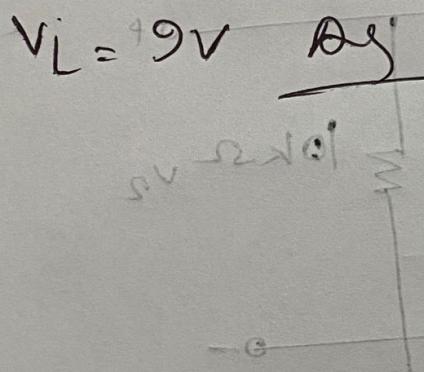\therefore In parallel case voltage are same



$$\therefore \frac{E}{R_1 + R_2} = \frac{E}{R_1} = I$$

$$A_{mr881.1} = \frac{15V}{100000 + 100} = 2E$$

$$(2E) \oplus (A_{mr881.1}) = V$$

$$2E \oplus 2E =$$

$$A_{81.0} = \frac{V_{81}}{100} = \frac{E}{R_1} = E$$