

5.3

7. For the series configuration, find

(a) Total resistance

(b) Total current

(c) Voltage across each resistive elements


(d) Hence, Total resistance, $R_T = (10 + 2 + 18)\Omega = 40\Omega$ (e) As per Ohm's Law, Current, $I_s = \frac{E}{R_T} = \frac{120}{40} A = 3A$

(f) Applying ohm's law in each resistive elements we can obtain voltage across each of them.

$$\text{So, } V_{R_1} = I_s R_1 = [(3A)(10\Omega)]V = 30V$$

$$V_{R_2} = I_s R_2 = [3A * 12\Omega]V = 36V$$
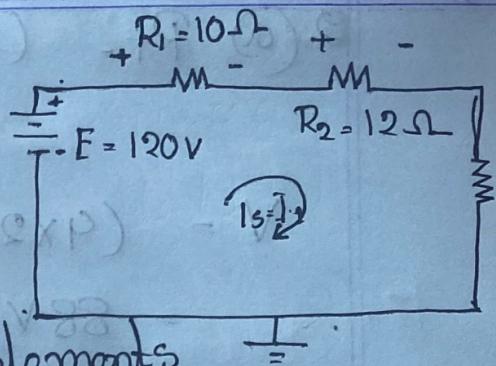
$$V_{R_3} = I_s R_3 = [18\Omega * 3A] = 54V$$



$$9. (a) R_T = (12 + 4 + 6) k\Omega$$

$$= 22 k\Omega$$


$$V = (4 \times 22)V$$

$$= 88V$$


$$(b) R_T = (18 + 14 + 8 + 40)\Omega = 80\Omega$$

$$V = \left(\frac{250}{1000} \times 80 \right) = 20V$$

10. (a) Force Power (a)

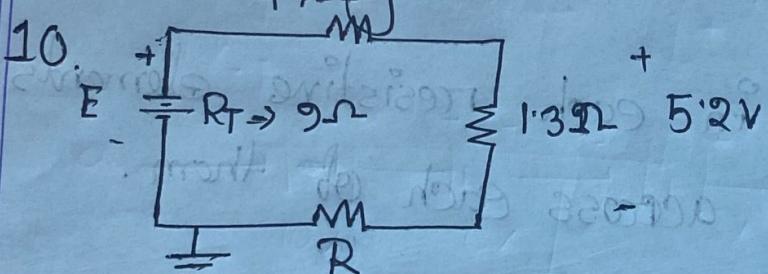


(a)

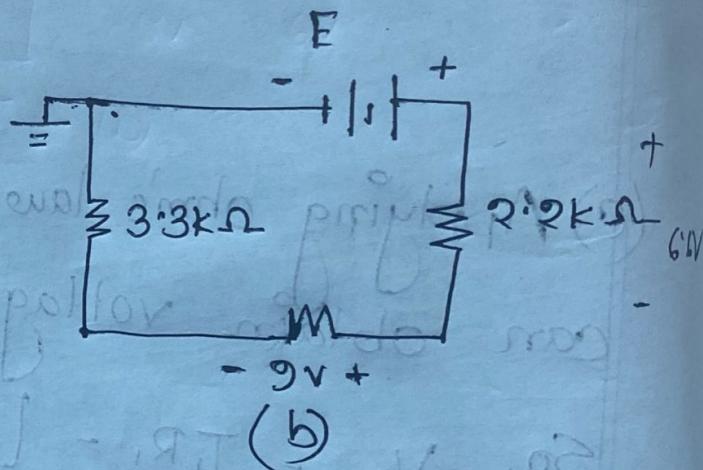

(b)


Hence Figure (b) can be drawn as

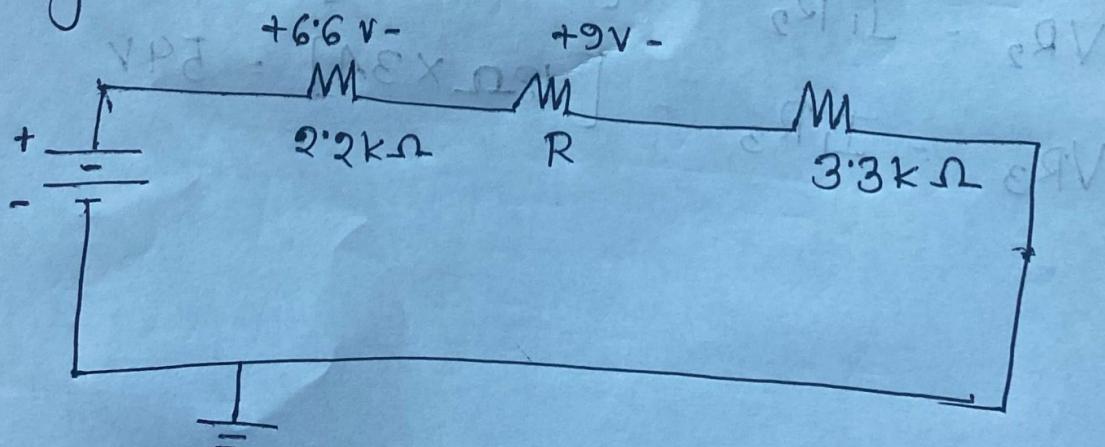

(a) For figure (a) Current $I = \frac{VR}{R} = \frac{5.2V}{1.3\Omega} = 4A$
 & for " (b) Current $I = \frac{VR}{R} = \frac{6.6V}{2.2k\Omega}$

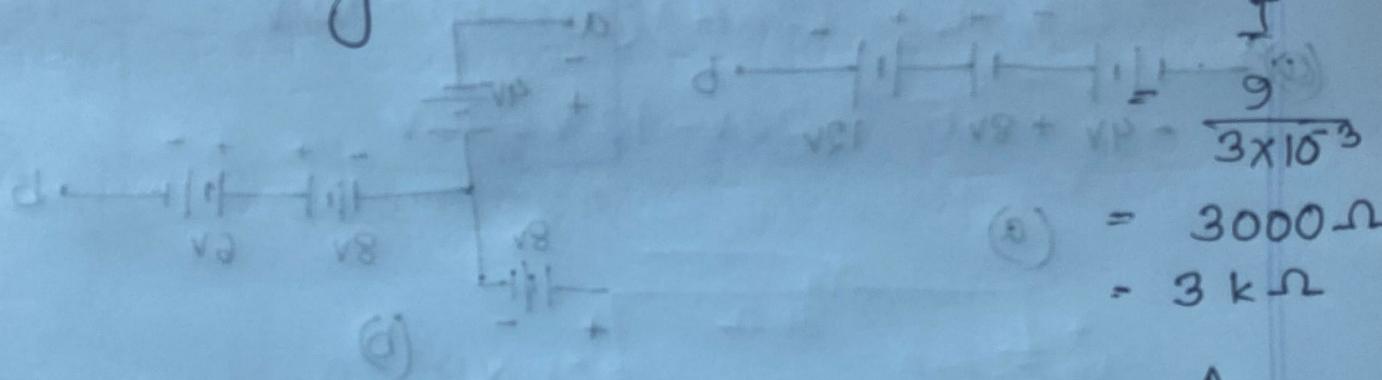
(b) For 1st Figure $IR_T = (4 \times 9)V = 36V$

For 2nd Figure, unknown Resistance, $R = \frac{V_{unk}}{I}$



$$R = \frac{36V}{I} = 3000\Omega = 3k\Omega$$


Ans

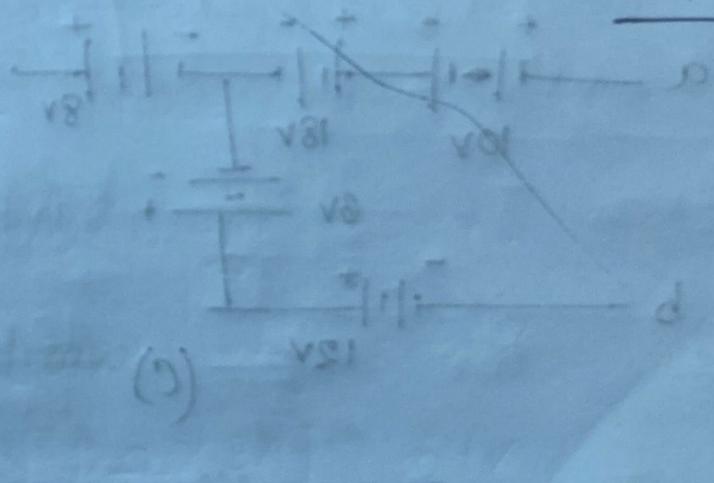


$$6(1) I = \frac{6.6}{2.2} = 3$$

$$\underline{5.5}$$

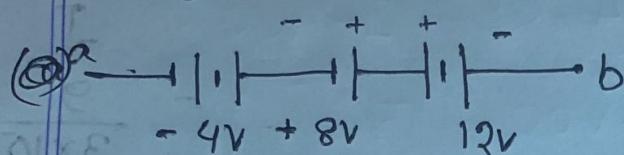
17. Combine the series voltage source into a single voltage source between points a & b



(a)

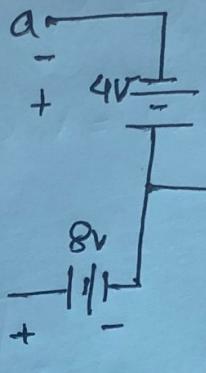

(b)

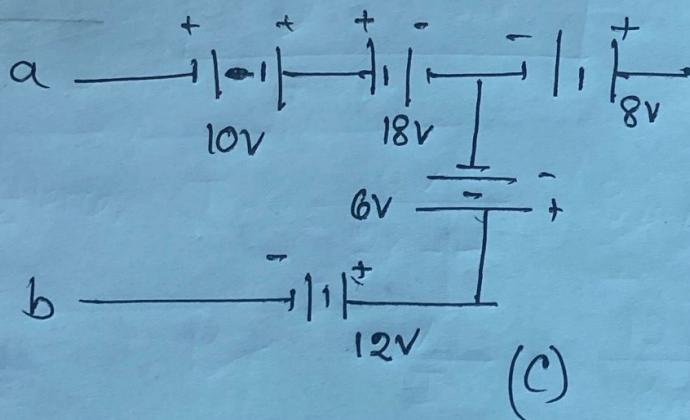


(c)

For Figure (a) $V_{ab} = -4V - 8V + 12V = 0$

For Figure (b) $V_{ab} = -4V - 8V + 6V = -6V$

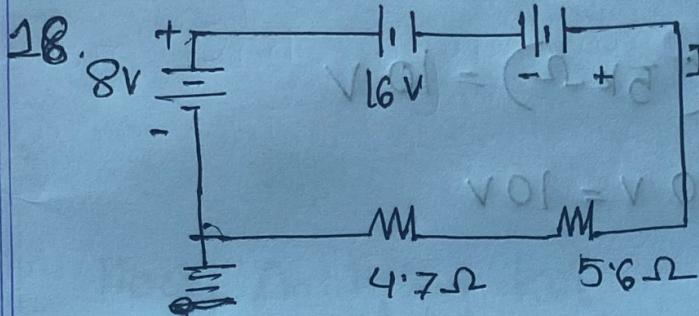For Figure (c) $V_{ab} = -10V + 18V - 6V + 12V = 14V$




$$V_S = -8 + 16 - 4 = 4V$$

$$R_T = 4.7 + 5.6 = 10.2\Omega$$

$$I = \frac{4}{10.2} = 0.392A$$

Single voltage drop across

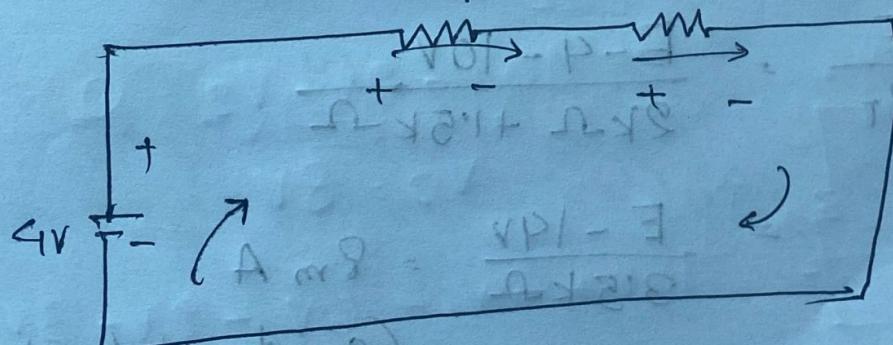

$$(4V + 10V) (A.m8) = P1 - E$$

$$VSP = E$$

Unknown Register


19. (a) $P = iR$

$$R = \frac{8mW}{I^2} = \frac{8mW}{(2mA)^2} = 2k\Omega$$

$$I = \frac{RE}{R_T} = \frac{20V - E}{3k\Omega + 2k\Omega} = 2mA \text{ (clockwise)}$$

$$\Rightarrow 20V - E = (2mA)(5k\Omega) = 10V$$

$$\therefore E = 20V - 10V = 10V$$

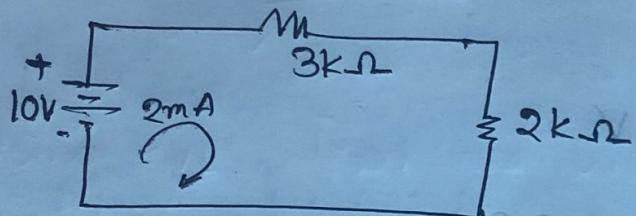

(b) Hence, $I = \frac{16V}{2k\Omega} = 8mA$


$$R = \frac{V}{I} = \frac{12V}{8mA} = 1.5k\Omega$$

$$I_S = \frac{E}{R_T} = \frac{E - 4 - 10V}{2k\Omega + 1.5k\Omega}$$

$$\Rightarrow \frac{E - 14V}{3.5k\Omega} = 8mA$$

$$\therefore E - 14 = (8mA)(3.5k\Omega)$$

$$\therefore E = 92V$$

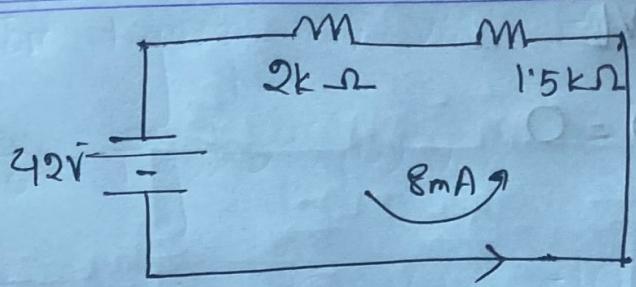

20. (a) ~~KVL~~

Here, Applying KVL

$$+10V - 4V - 3V - V = 0$$

$$\therefore V = 14V - 3V = 11V$$

(b) Applying KVL,


$$+30V + 20V - 8V - V = 0$$

$$\therefore V = 50V - 8V = 42V$$

(c) Applying KVL

$$+16V - 10V - 4V - V + 60V = 0$$

$$\therefore V = 62V$$

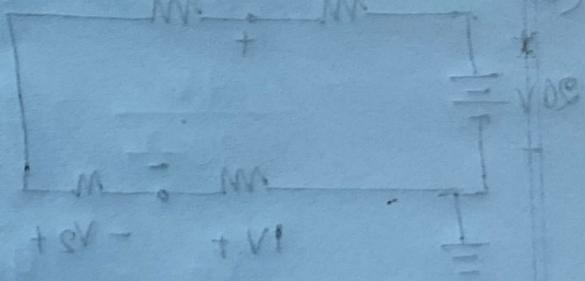

21. (a) Hence Applying KVL

$$60 - 12 - V - 20 = 0$$

$$\therefore V = 28V$$

(b) Hence, Applying KVL


$$V + 18 - 14 - 6 - 2 = 0$$

$$\therefore V = 4 = 0$$

$$\therefore V = 4$$

Ams


23 Using KVL, Find the unknown voltage

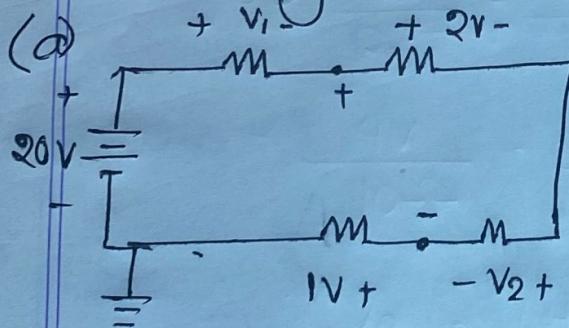

Applying KVL

$$+20V - V_1 - 10V - 4V = 0$$

$$V_1 = 9V \therefore$$

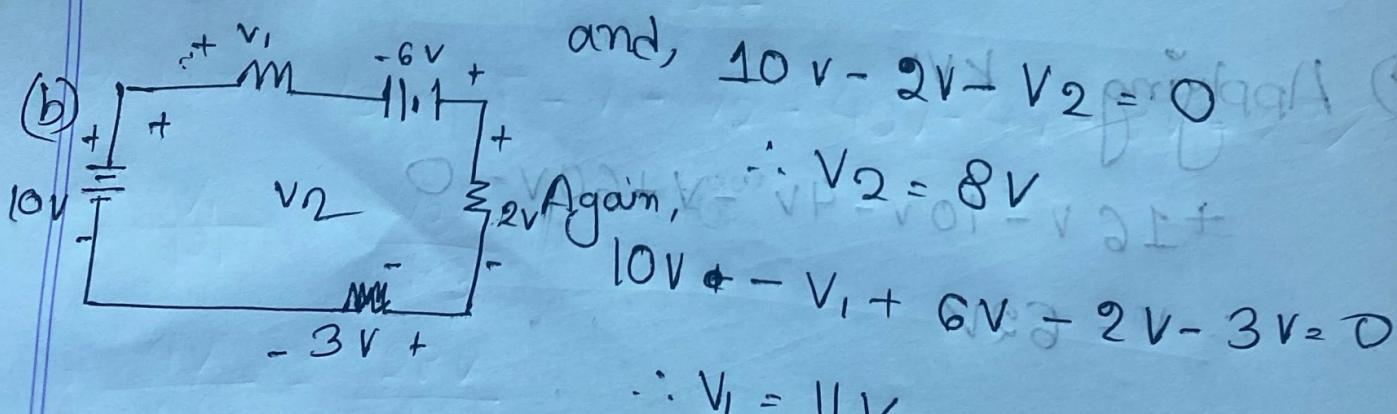


Again,

$$10V - V_2 - 3V = 0 \therefore V_2 = 7V$$

5.7

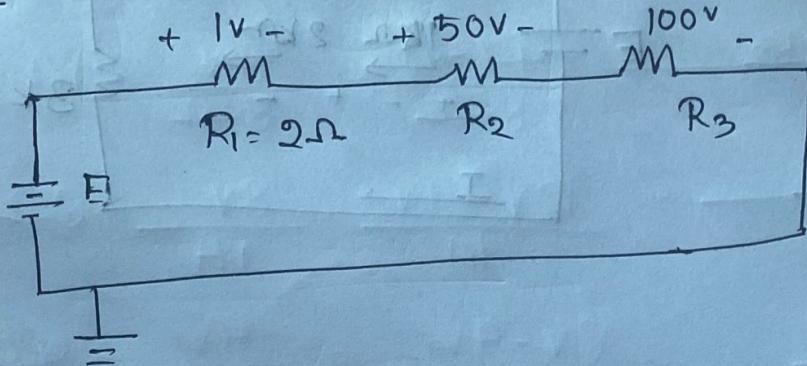24. Determine the values of unknown resistances,



$$\text{Here, } \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$\Rightarrow \frac{1V}{2\Omega} = \frac{50V}{R_2}$$

$$\therefore R_2 = \frac{(50V)(2\Omega)}{1V} = 100\Omega$$

$$\text{Again, } \frac{V_1}{R_1} = \frac{V_3}{R_3}$$

$$\frac{1V}{2\Omega} = \frac{100V}{R_3}$$

$$\therefore R_3 = \frac{(100V)(2\Omega)}{1V} = 200\Omega$$

$$\frac{V_1}{R_1} = \frac{V}{1\Omega}$$

$$\frac{V_2}{R_2} = \frac{V}{2\Omega}$$

$$\frac{V_3}{R_3} = \frac{V}{4\Omega}$$

28. Hence,

$$\frac{2}{1} = \frac{V_2}{2}$$


$$\Rightarrow V_2 = 4V$$

$$\text{and } \frac{2}{1} = \frac{V_4}{3}$$

$$\Rightarrow V_4 = 6V$$

$$I = \frac{2}{1} = 2mA$$
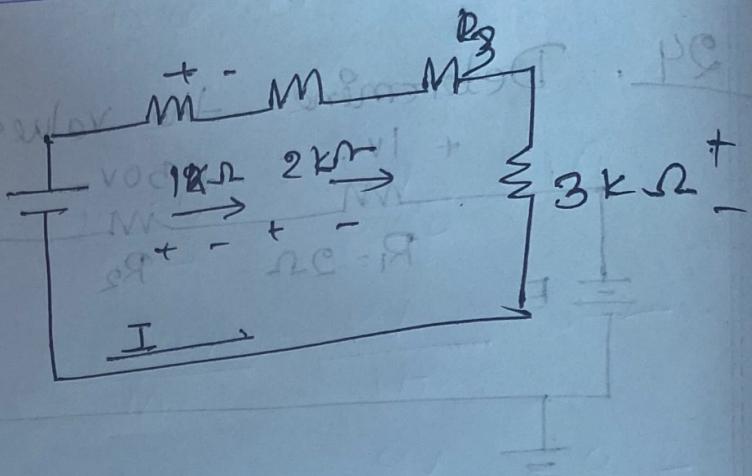
$$\begin{aligned} \text{and } E &= 2+4+12+6 \\ &= 24V \end{aligned}$$




30

$$\text{Hence } \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$= \frac{4V}{10\Omega} = \frac{V_2}{20\Omega}$$

$$\therefore V_2 = \frac{(4V)(20\Omega)}{10\Omega} = 8V$$

$$(20\Omega)(4V) = 8V \therefore$$

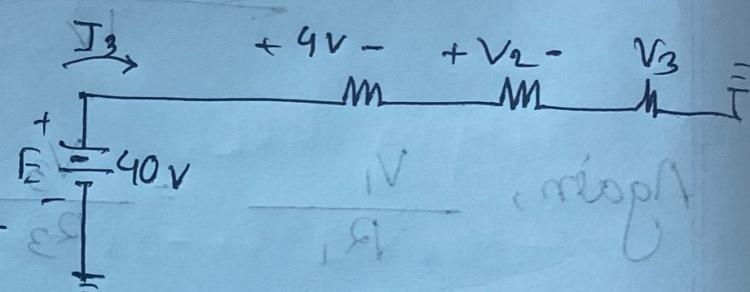

(b)

$$\text{Hence, } V_3 = E - V_1 - V_2 = 40V - 4V - 8V = 28V$$

$$\textcircled{c} \quad \frac{V_1}{R_1} = \frac{V_3}{R_3}$$

$$\therefore \frac{4V}{10\Omega} = \frac{28V}{R_3}$$

$$\Rightarrow R_3 = \frac{(28V)(10\Omega)}{4V} = 70\Omega$$

Q 5.9 ~~concerned to level off drift~~

36. Determine current I (with direction) & voltage V (with polarity) for the following figure

For Figure (a)

$$\text{Hence } V = 80V - 26V = 54V$$

$$\& R_T = 6\Omega + 3\Omega = 9\Omega$$

$$\therefore I = \frac{54V}{9\Omega} = 6A \& V = IR = (6A)(3\Omega) = 18V$$

The direction would be clock wise as $80V > 26V$

For Figure (b)


$$E = 70V - 10V = 60V$$

$$R_T = 10\Omega + 20\Omega + 30\Omega = 60\Omega$$

$$\therefore I = \frac{E}{R_T} = \frac{60V}{60\Omega} = 1A$$

Direction is clock wise
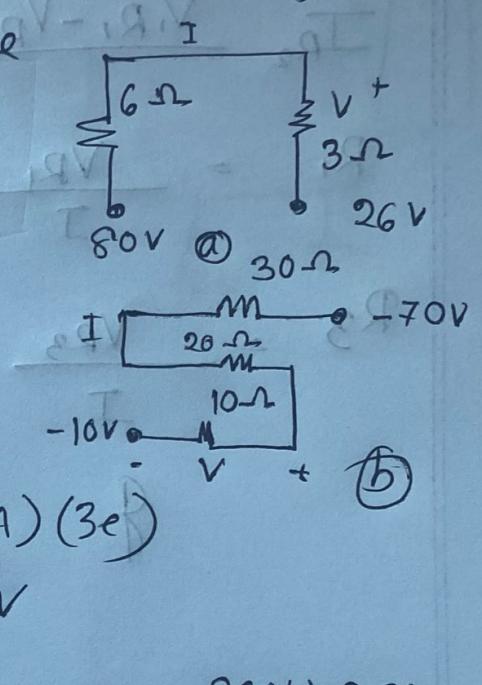
$$\text{Again, } V, IR (1A) (10\Omega) = 10V$$




39. Find the level of Resistance R_1 & R_3

As per Law,

$$I_{R_2} = \frac{V_{R_1} - V_{R_2}}{R_2} = \frac{4 - (-4)}{8\Omega} = \frac{8V}{8\Omega} = 1A$$

$$R_1 = \frac{V_{R_1}}{I} = \frac{12V - 4V}{1A} = \frac{8V}{1A} = 8\Omega$$
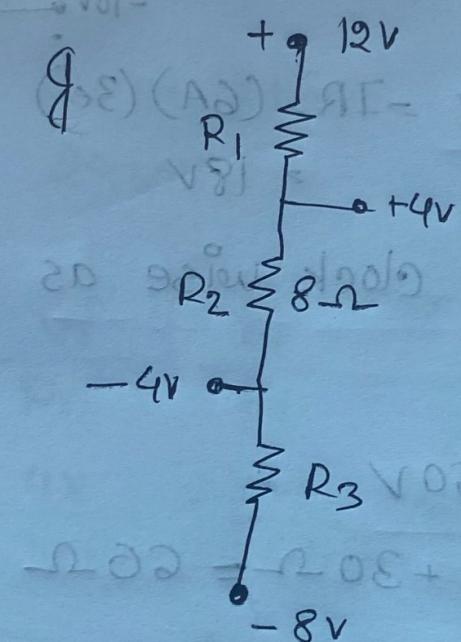
$$R_3 = \frac{V_{R_3}}{I} = \frac{8V - 4V}{1A} = \frac{4V}{1A} = 4\Omega$$



$$AI = \frac{E}{R_{eq}} = \frac{12V}{20\Omega} = \frac{12}{20} = 0.6A$$

$$V_{01} = (-20V) (0.6) = -12V$$

Q2 Determine $V_0, V_4, V_7, V_{10}, V_{23}, V_{30}$

V_{67}, V_{56} and I (magnitude & direction)

Here, $V_0 = 0V$ (ground)

$$\begin{aligned} V_4 &= -V_1 - 2V \\ &= -(6 \text{ mA} \times 2 \text{ k}\Omega) - 2V \\ &= 12V - 2 \\ &= 10V \end{aligned}$$

$$V_7 = 4V$$

$$V_{10} = 20V - 0V = 20V$$

$$V_{23} = -2V + 8V = 6V$$

$$V_{30} = -8V - 0V = -8V$$

$$V_{67} = 4V - 0V = 4V$$

$$V_{56} = -2V - 4V = -6V$$

Here, Current $I = \frac{V_{23}}{4\Omega} = \frac{6V}{4\Omega} = 1.5A$ &

& the direction is clockwise (↑)

