



NORTH SOUTH UNIVERSITY
DEPARTMENT OF ELECTRICAL & COMPUTER
ENGINEERING

Assignment-2

Summer 2022

EEE141: Electrical Circuits I

Section: 08

Name: Mosroor Mofiz Arman

ID: 1921079642

Submitted to:

Syeda Sarita Hassan (SSH1)


Lecturer

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Date: 18-08-2022

Chapter - 08

Example

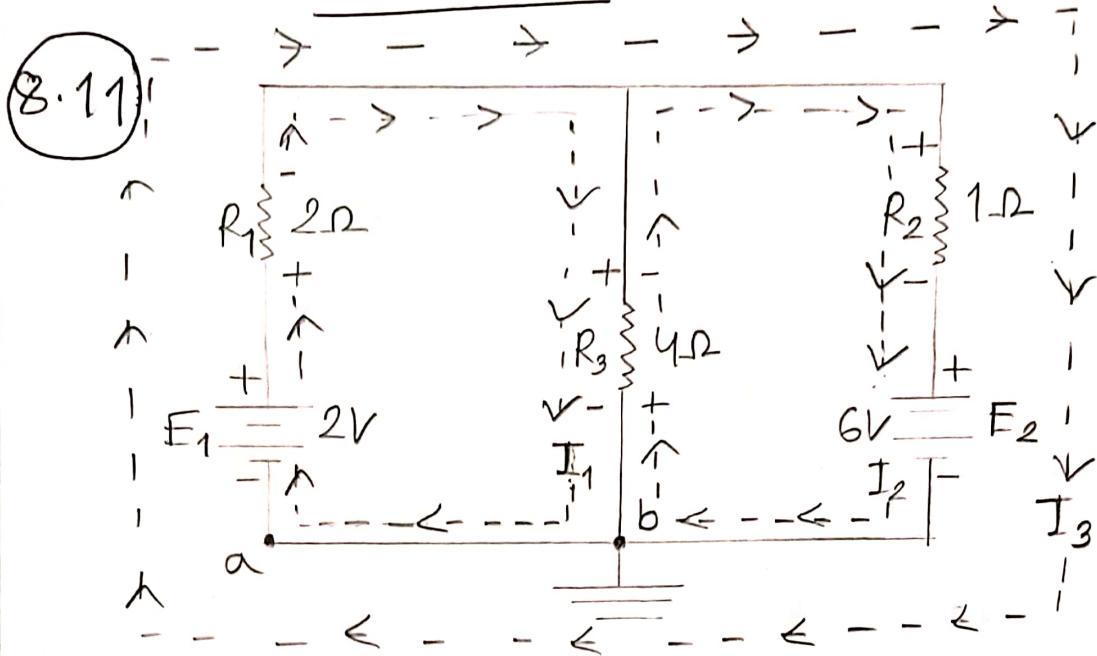

Loop 1°

$$E_1 - V_1 - V_3 = 0$$

$$\Rightarrow 2 - 2 \cdot I_1 - 4 \cdot (I_1 - I_2) = 0$$

$$\Rightarrow 2 - 2I_1 - 4I_1 + 4I_2 = 0,$$

$$\Rightarrow -6I_1 + 4I_2 = -2$$

$$\Rightarrow 6I_1 - 4I_2 = 2 \dots \dots \text{(i)}$$

Loop 2°

$$-V_3 - V_2 - E_2 = 0.$$

$$\Rightarrow -4 \cdot (I_2 - I_1) - 1 \cdot I_2 - 6 = 0,$$

$$\Rightarrow -4I_2 + 4I_1 - I_2 - 6 = 0,$$

$$\Rightarrow 4I_1 - 5I_2 = 6 \dots \dots \text{(ii)}$$

From (i) and (ii),

$$6I_1 - 4I_2 = 2$$

$$4I_1 - 5I_2 = 6.$$

$$\therefore I_1 = -1A \quad \text{and} \quad I_2 = -2A.$$

From loop 1, $I_{R_3} = I_1 - I_2$


$$\Rightarrow I_{4,2} = I_1 - I_2 = -1A + 2A$$

$$\Rightarrow I_{4,2} = 1A \downarrow$$

$\therefore I_{4,2} = 1A$ (in the direction of I_1)

(Ans).

8.12

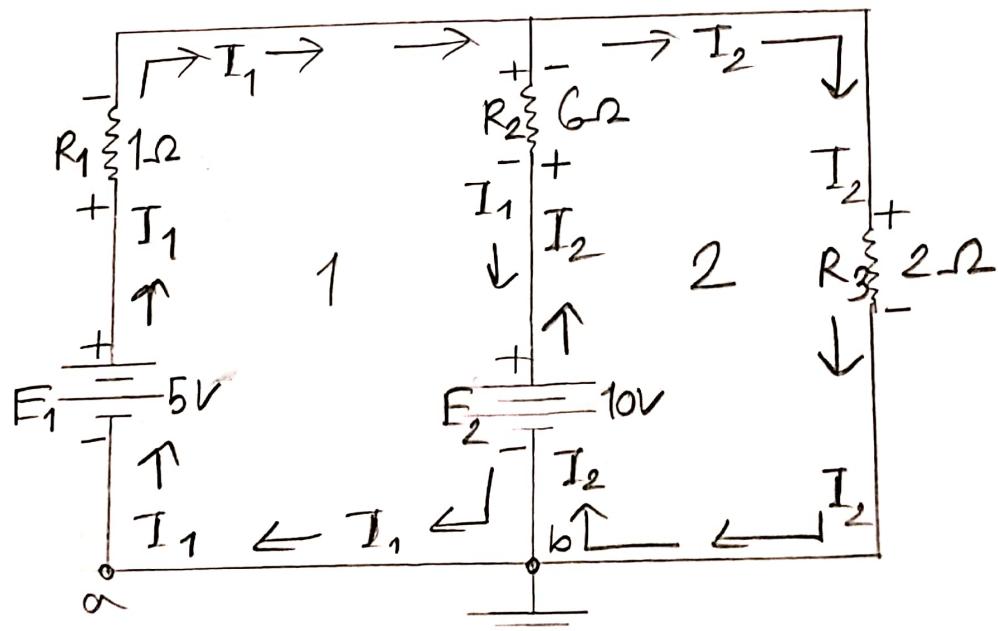

$$\text{loop 1: } E_1 - V_1 - V_2 - E_2 = 0$$

$$\Rightarrow E_1 - 1 \cdot I_1 - 6 \cdot (I_1 - I_2) - E_2 = 0.$$

$$\Rightarrow 5 - I_1 - 6I_1 + 6I_2 - 10 = 0.$$

$$\Rightarrow -7I_1 + 6I_2 = 5 \dots \dots \dots \text{(i)}$$

Loop 2 : $E_2 - V_2 - V_3 = 0$

$$\Rightarrow 10 - 6(I_2 - I_1) - 2 \cdot I_2 = 0.$$

$$\Rightarrow 10 - 6I_2 + 6I_1 - 2I_2 = 0.$$

$$\Rightarrow 6I_1 - 8I_2 = -10$$

$$\Rightarrow -6I_1 + 8I_2 = 10 \dots \dots \dots \text{(ii)}$$

From (i) and (ii),

$$-7I_1 + 6I_2 = 5$$

$$-6I_1 + 8I_2 = 10$$

$$\therefore I_1 = 1A \quad \text{and} \quad I_2 = 2A.$$


Since $I_2 > I_1$, from Loop 2, $I_{R_2} = I_2 - I_1$

$$\Rightarrow I_{G-2} = 2A - 1A = 1A \uparrow$$

$\therefore I_{G-2} = 1A$ (in the direction of I_2).

(Ans.)

8.13

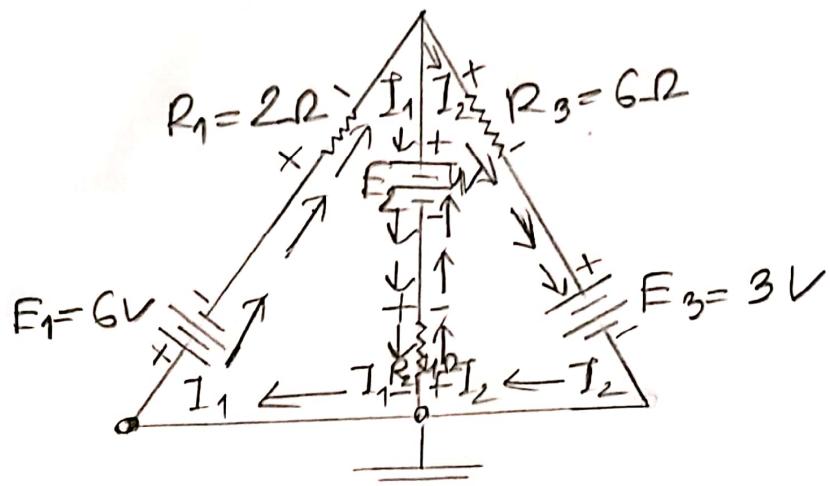

$$\text{loop 1} : -E_1 - V_1 - E_2 - V_2 = 0.$$

$$\Rightarrow -6 - 2 \cdot I_1 - 4 - 4 \cdot (I_1 - I_2) = 0$$

$$\Rightarrow -6 - 2I_1 - 4 - 4I_1 + 4I_2 = 0.$$

$$\Rightarrow -6I_1 + 4I_2 = 10 \dots \text{(i)}$$

$$\text{loop 2} : -V_2 + E_2 - V_3 - E_3 = 0.$$

$$\Rightarrow -4(I_2 - I_1) + 4 - 6 \cdot I_2 - 3 = 0.$$

$$\Rightarrow -4I_2 + 4I_1 - 6I_2 + 1 = 0.$$

$$\Rightarrow 4I_1 - 10I_2 = -1. \dots \text{(ii)}$$

From (i) and (ii),

$$-6I_1 + 4I_2 = 10$$

$$4I_1 - 10I_2 = -1$$

$$\therefore I_1 = -2.18 \text{ A} \quad \text{and} \quad I_2 = -0.22 \text{ A}$$

C.


Since $I_2 > I_1$, from loop 2, $I_{R_2} = I_2 - I_1$

$$\Rightarrow I_{4-2} = -0.77A + 2.18A = 1.41A \uparrow$$


$\therefore I_{4-2} = 1.41A$ (in the direction of I_2)

(Ans).

8.14

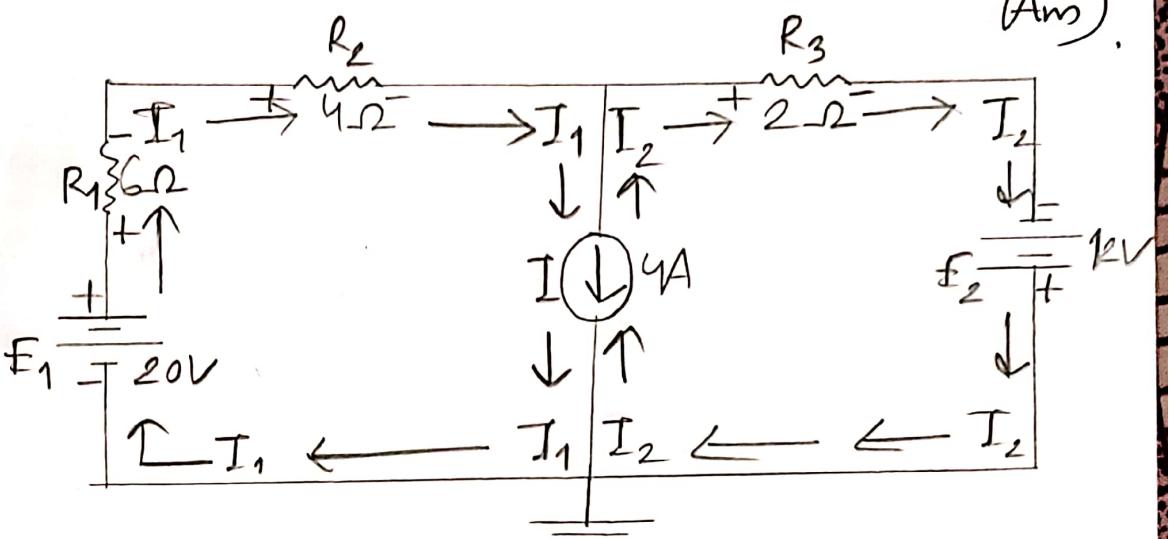

Defining the supermesh current,

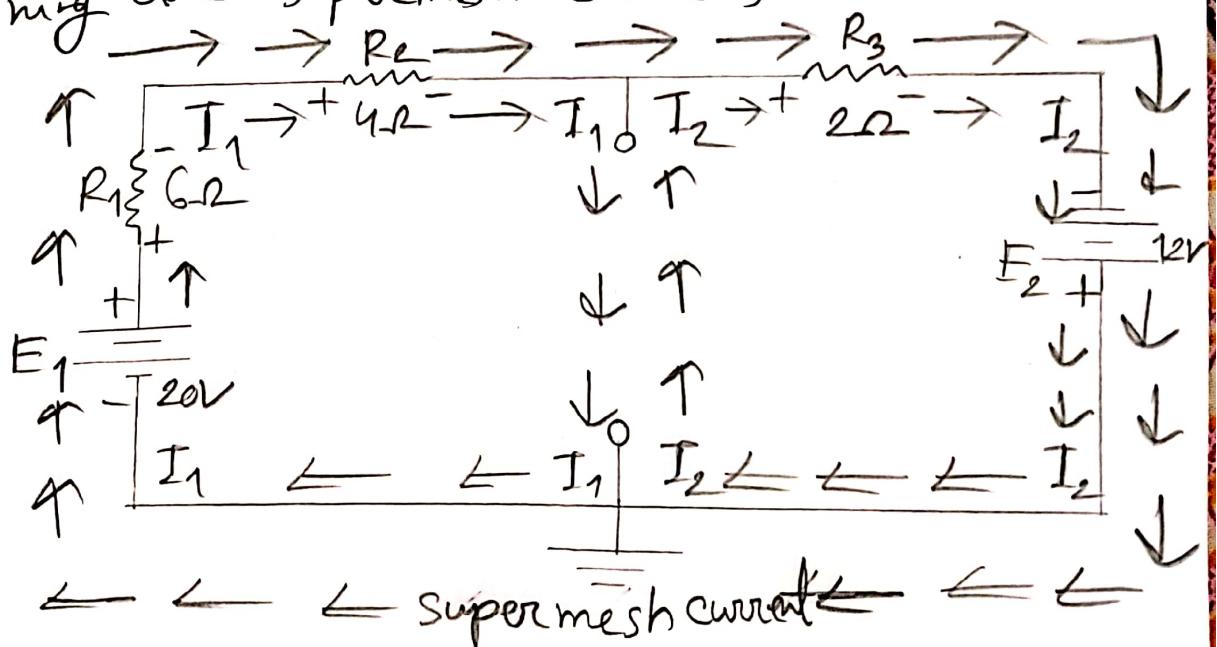

Here,

$$E_1 - R_1 - R_2 - R_3 + E_2 = 0.$$

$$\Rightarrow 20 - 6I_1 - 4I_1 - 2I_2 + 12 = 0.$$

$$\Rightarrow -10I_1 - 2I_2 = -32 \dots \dots \dots \text{(i)}$$

Again,

$$I_1 - I_2 = 4 \dots \dots \dots \text{(ii)}$$

From (i) and (ii),

$$-10I_1 - 2I_2 = -32$$


$$I_1 - I_2 = 4$$

$$\therefore I_1 = 3.33 A \downarrow \text{ and } I_2 = -0.67 A$$


$$\therefore I_2 = 0.67 A \uparrow$$

(Ans).

8.15

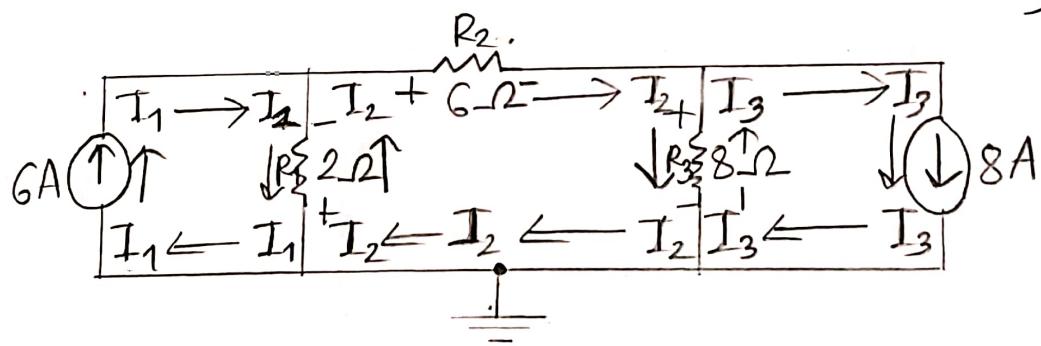

Defining the Supermesh current,

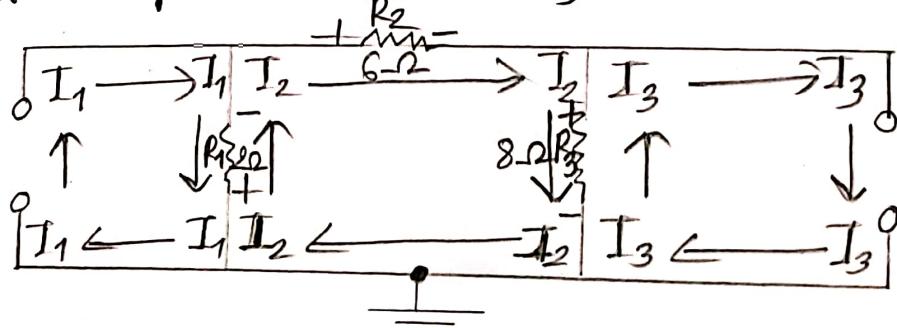

Here,

$$-V_1 - V_2 - V_3 = 0$$

$$\Rightarrow 2(I_2 - I_1) - 6I_2 - 8(I_2 - I_3) = 0.$$

$$\Rightarrow -2I_2 + 2I_1 - 6I_2 - 8I_2 + 8I_3 = 0$$

$$\Rightarrow 2I_1 - 16I_2 + 8I_3 = 0 \dots \dots \text{(i)}$$

Again,

$$I_1 = 6A \dots \dots \text{(ii)}$$

$$I_3 = 8A \dots \dots \text{(iii)}$$

From (i), (ii) and (iii),

$$2(6) - 16I_2 + 8(8) = 0$$

$$\Rightarrow -16I_2 + 76 = 0$$

$$\Rightarrow I_2 = \frac{76}{16}$$


$$\therefore I_2 = 4.75A.$$

$$\therefore I_{R_1} = I_{2-2} = I_1 - I_2 = (6 - 4.75) = 1.25A \downarrow$$

$$\therefore I_{R_3} = I_{8-2} = I_3 - I_2 = (8 - 4.75) = 3.25A \uparrow$$

(Ans)

(8.16)

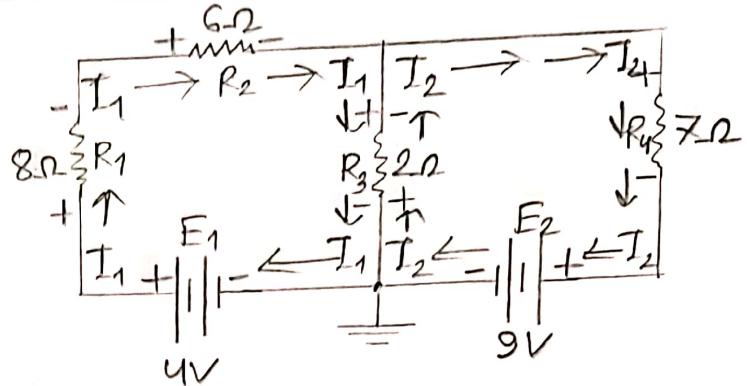

Loop 1 :

$$\begin{aligned}
 & E_1 - V_1 - V_2 - V_3 = 0 \\
 \Rightarrow & 4 - 8I_1 - 6I_1 - 2(I_1 - I_2) = 0 \\
 \Rightarrow & 4 - 14I_1 - 2I_1 + 2I_2 = 0 \\
 \Rightarrow & -16I_1 + 2I_2 = -4 \\
 \Rightarrow & 16I_1 - 2I_2 = 4 \quad \dots \dots \dots \text{(i)}
 \end{aligned}$$

Loop 2 :


$$\begin{aligned}
 & -V_3 - V_4 - E_2 = 0 \\
 \Rightarrow & -2(I_2 - I_1) - 7I_2 - 9 = 0 \\
 \Rightarrow & -2I_2 + 2I_1 - 7I_2 - 9 = 0 \\
 \Rightarrow & 2I_1 - 9I_2 = 9 \quad \dots \dots \dots \text{(ii)}
 \end{aligned}$$

From (i) and (ii),

$$\begin{aligned}
 & 16I_1 - 2I_2 = 4 \\
 & 2I_1 - 9I_2 = 9 \\
 \therefore & I_1 = 0.129A \quad \text{and} \quad I_2 = -0.971A
 \end{aligned}$$

$$\begin{aligned}
 & I_{R_2} = I_{R_4} = I_2 = -0.971A = 0.971A \uparrow \\
 & (\text{Ans})
 \end{aligned}$$

8-17

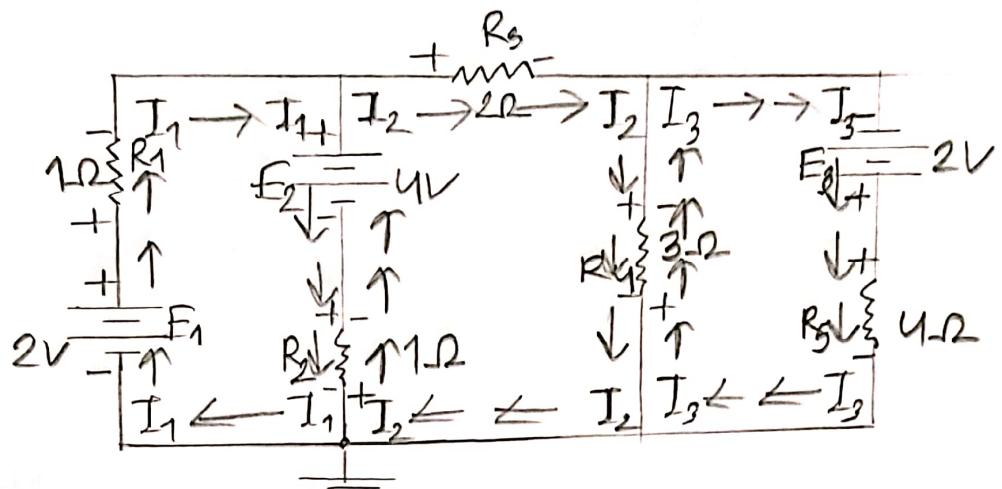

Loop 1 :

$$\frac{1}{E_1 - V_1 - E_2 - V_2} = 0.$$

$$\Rightarrow 2 - 1 \cdot I_1 - 4 - 1 \cdot (I_1 - I_2) = 0.$$

$$\Rightarrow -I_1 - 2 - I_1 + I_2 = 0.$$

Loop 2:

$$\overline{E_2} - V_3 - V_4 - V_2 = 0$$

$$\Rightarrow y - 2I_2 - 3(I_2 - I_3) - 1(I_2 - I_1) = 0.$$

$$4 - 2I_2 - 3I_2 + 3I_3 - I_2 + I_1 = 0$$

$$\Rightarrow I_1 - 6I_2 + 3I_3 = -4 \quad \dots \dots \text{(ii)}$$

Loop 3 :

$$\overline{E_3} - V_5 - N_y = 0$$

$$\Rightarrow 2I_1 - 4I_3 + 3(I_3 - I_2) = 0$$

$$\Rightarrow 2I_3 - 4I_3 + 3I_3 + 3I_2 = 0$$

$$\Rightarrow 3I_2 - 8I_3 = -2. \quad \dots \text{ (iii)}$$

From (i), (ii), (iii),

$$-2I_1 + I_2 = 2$$

$$I_1 - 6I_2 + 3I_3 = -4$$


$$3I_2 - 7I_3 = -2$$

$$\therefore I_1 = -0.542A, I_2 = 0.915A, I_3 = 0.678A$$

$$\therefore I_1 = 0.542A \uparrow, I_2 = 0.915A \downarrow, I_3 = 0.678A \downarrow$$

(Ans)

8.18

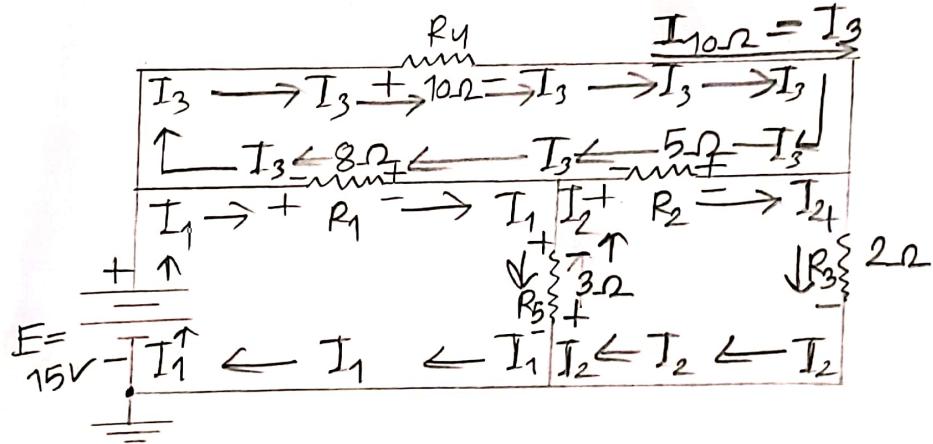

Loop 1:

$$\begin{aligned}
 E - V_1 - V_5 &= 0 \\
 \Rightarrow 15 - 8(I_1 - I_3) - 3(I_1 - I_2) &= 0 \\
 \Rightarrow 15 - 8I_1 + 8I_3 - 3I_1 + 3I_2 &= 0 \\
 \Rightarrow -11I_1 + 3I_2 + 8I_3 &= -15 \quad \dots \dots \dots \text{(i)}
 \end{aligned}$$

Loop 2:

$$\begin{aligned}
 -V_3 + V_5 + V_6 &= 0 \\
 \Rightarrow 2I_2 + 3(I_2 - I_1) + 5(I_2 - I_3) &= 0 \\
 \Rightarrow 2I_2 + 3I_2 - 3I_1 + 5I_2 - 5I_3 &= 0
 \end{aligned}$$

$$\Rightarrow 3I_1 + 10I_2 - 5I_3 = 0 \dots \dots \dots \text{(ii)}$$

Loop 3 :

$$V_4 + V_2 + V_1 = 0$$

$$\Rightarrow 10I_3 + 5(I_3 - I_2) + 8(I_3 - I_1) = 0.$$

$$\Rightarrow 10I_3 + 5I_3 - 5I_2 + 8I_3 - 8I_1 = 0$$

$$\Rightarrow -8I_1 - 5I_2 + 23I_3 = 0 \dots \dots \dots \text{(iii)}$$

From (i), (ii), (iii),

$$-11I_1 + 3I_2 + 8I_3 = -15$$


$$-3I_1 + 10I_2 - 5I_3 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0.$$

$$\therefore I_1 = 2.63 A \downarrow, I_2 = 1.3998 A \downarrow, I_3 = 1.22 A \downarrow$$

$$\therefore I_{10-2} = I_{R_4} = I_3 = 1.22 A \downarrow \quad (\text{Ans})$$

8.20

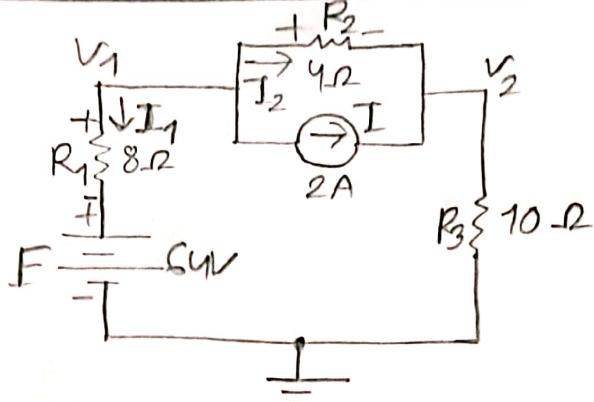

For node V_1 ,

$$I_1 + I_2 + I = 0.$$

$$\Rightarrow \frac{V_1 - E}{R_1} + \frac{V_1 - V_2}{R_2} + 2 = 0.$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{E}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2} + 2 = 0.$$


$$\Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_2}{R_2} = \frac{E}{R_1} - 2$$

$$\Rightarrow V_1 \left(\frac{1}{8} + \frac{1}{4} \right) - \frac{V_2}{4} = \frac{64}{8} - 2$$

$$\Rightarrow \frac{3V_1}{8} - \frac{V_2}{4} = 6$$

$$\Rightarrow 0.375V_1 - 0.25V_2 = 6 \quad \dots \dots \text{(i).}$$

For node V_2 ,

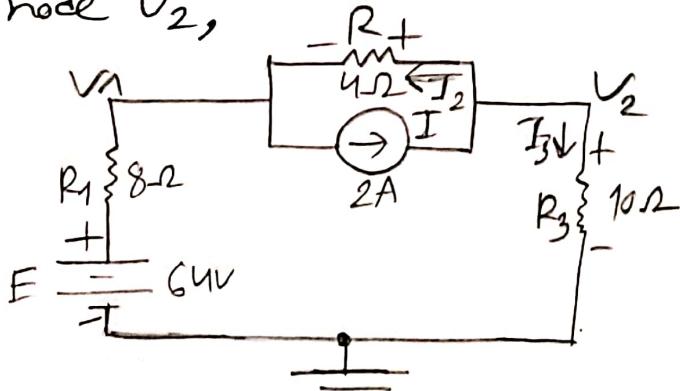

$$I = I_2 + I_3$$

$$\Rightarrow 2 = \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3}$$

$$\Rightarrow 2 = \frac{V_2}{R_2} - \frac{V_1}{R_2} + \frac{V_2}{R_3}$$

$$\Rightarrow V_2 \left(\frac{1}{4} + \frac{1}{10} \right) - \frac{V_1}{8} = 2$$

$$\Rightarrow \frac{7V_2}{20} - \frac{V_1}{8} = 2$$

$$\Rightarrow 0.35V_2 - 0.25V_1 = 2 \quad \dots \dots \text{(ii)}$$

From (i) & (ii),

$$0.35V_1 - 0.25V_2 = 6$$

$$-0.25V_1 + 0.35V_2 = 2$$


$$\therefore V_1 = 37.82V \quad \text{and} \quad V_2 = 32.73V$$

$$\text{Since } E > V_1, \quad I_{R_1} = \frac{E - V_1}{R_1} = \frac{64 - 37.82}{8} A \\ = 3.27A \uparrow$$

$$I_{R_3} = \frac{V_{R_3}}{R_3} = \frac{V_2}{R_3} = \frac{32.73}{10} = 3.27A \downarrow$$


$$\text{Since } V_1 > V_2, \quad I_{R_2} = \frac{V_1 - V_2}{R_2} = \frac{37.82 - 32.73}{4} A \\ = 1.27A \uparrow$$

(Ans.)

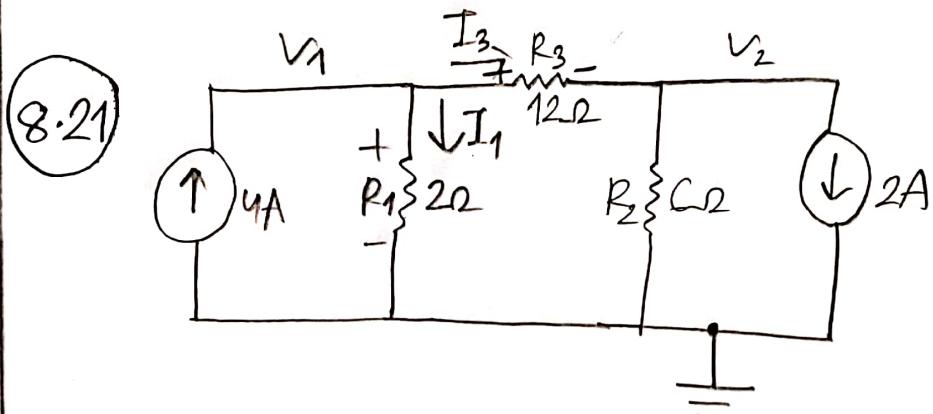

For node V_1 ,
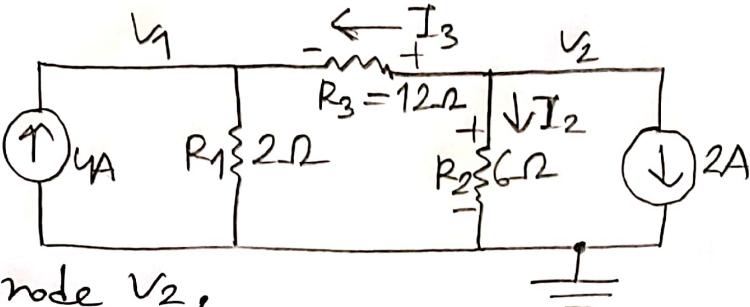
$$\begin{aligned}
 V &= I_1 + I_3 \\
 \Rightarrow V &= \frac{V_1 - 0}{R_1} + \frac{V_1 - V_2}{R_3} \\
 \Rightarrow V &= \frac{V_1}{2} + \frac{V_1}{12} - \frac{V_2}{12} \\
 \Rightarrow 0.583V_1 - 0.083V_2 &= V \dots \text{(i)}
 \end{aligned}$$



For node V_2 ,

$$\begin{aligned}
 I_3 + I_2 + 2 &= 0 \\
 \Rightarrow \frac{V_2 - V_1}{R_3} + \frac{V_2 - 0}{R_2} + 2 &= 0 \\
 \Rightarrow \frac{V_2}{12} - \frac{V_1}{12} + \frac{V_2}{6} + 2 &= 0 \\
 \Rightarrow -0.083V_1 + 0.25V_2 &= -2 \dots \text{(ii)}
 \end{aligned}$$

From (i) and (ii),

$$\begin{aligned}
 0.583V_1 - 0.083V_2 &= 4 \\
 -0.083V_1 + 0.25V_2 &= -2
 \end{aligned}$$

$$\therefore V_1 = 6V \quad \text{and} \quad V_2 = -6V$$


$$\text{Since } V_1 > V_2, I_{R_3} = \frac{V_1 - V_2}{R_3} = \frac{6 - (-6)}{12} A = 1A \uparrow$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_1}{R_1} = \frac{6V}{2\Omega} = 3A \downarrow$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_2}{R_2} = \frac{-6V}{6\Omega} = 1A \uparrow$$

(Ans).

8.23

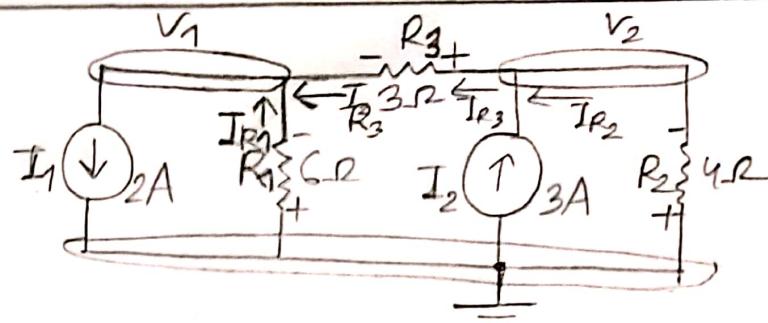

$$I_{R_1} + I_{R_3} = I_1$$

$$\Rightarrow \frac{V_1 - 0}{R_1} + \frac{V_1 - V_2}{R_3} = 2$$

$$\Rightarrow \frac{V_1}{6} + \frac{V_1}{3} - \frac{V_2}{3} = 2 \quad \text{(i)}$$

$$\Rightarrow \frac{V_1}{2} - \frac{V_2}{3} = 2 \quad \text{(i)}$$

$$I_{R_2} + I_2 = I_{R_3}$$

$$\Rightarrow \frac{V_2 - 0}{R_2} + 3 = \frac{V_1 - V_2}{R_3} \quad \text{(ii)}$$

$$\Rightarrow \frac{V_2}{4} - \frac{V_1}{3} + \frac{V_2}{3} = -3$$

$$\Rightarrow -\frac{V_1}{3} + \frac{7V_2}{12} = -3 \quad \text{(ii)}$$

From (i) & (ii),


$$0.5V_1 - 0.33V_2 = 2$$

$$-0.33V_1 + 0.583V_2 = -3$$

$$\therefore V_1 = 0.964V \quad \text{and} \quad V_2 = -4.6V$$

(Ans)

8.24)

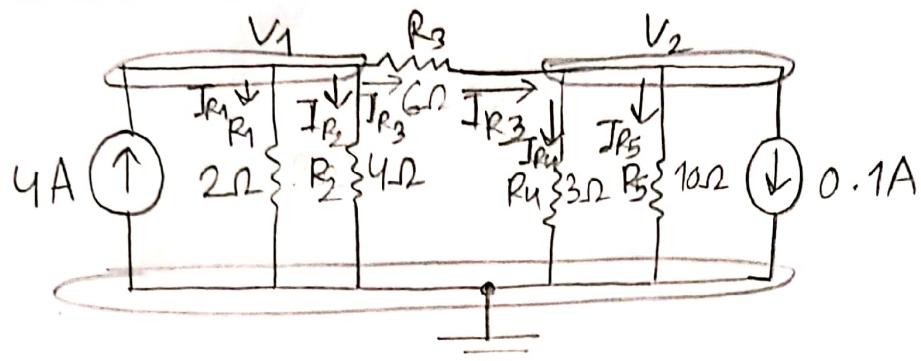

$$\begin{aligned}
 4 &= I_{R1} + I_{R2} + I_{R3} \\
 \Rightarrow 4 &= \frac{V_1 - 0}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_3} \\
 \Rightarrow 4 &= \frac{V_1}{2} + \frac{V_1}{4} + \frac{V_1}{6} - \frac{V_2}{6} \\
 \Rightarrow \frac{11V_1}{12} - \frac{V_2}{6} &= 4 \dots \text{(i)}
 \end{aligned}$$

$$\begin{aligned}
 0.1 + I_{R5} + I_{R4} &= I_{R3} \\
 \Rightarrow 0.1 + \frac{V_2 - 0}{R_5} + \frac{V_2 - 0}{R_4} &= \frac{V_1 - V_2}{R_3} \\
 \Rightarrow 0.1 + \frac{V_2}{10} + \frac{V_2}{3} &= \frac{V_1}{6} - \frac{V_2}{6} \\
 \Rightarrow 0.1 + \frac{V_2}{10} + \frac{V_2}{3} - \frac{V_1}{6} + \frac{V_2}{6} &= 0 \\
 \Rightarrow \frac{V_1}{6} - \frac{3V_2}{5} &= 0.1 \dots \text{(ii)}
 \end{aligned}$$

From (i) and (ii),


$$0.9167V_1 - 0.167V_2 = 4$$

$$0.167V_1 - 0.6V_2 = 0.1$$

$$\therefore V_1 = 4.56V \quad \text{and} \quad V_2 = 1.103V$$

(Ans).

8.25

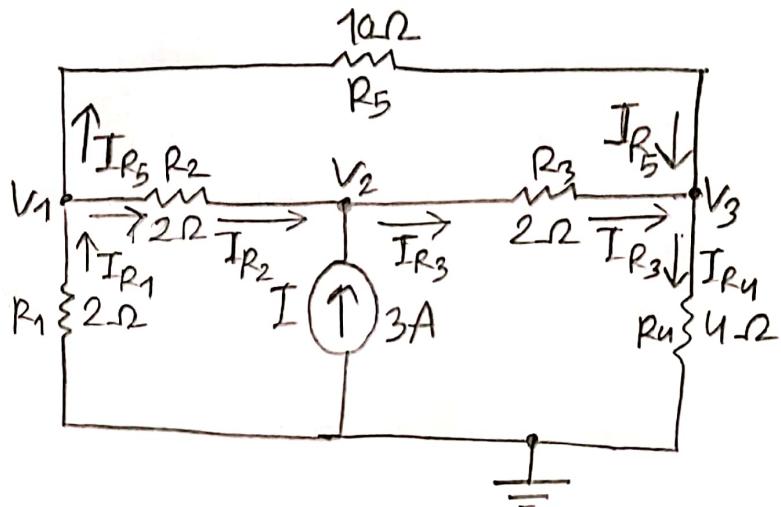

$$\begin{aligned}
 I_{R1} &= I_{R2} + I_{R5} \\
 \Rightarrow \frac{0 - V_1}{R_1} &= \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_3}{R_5} \\
 \Rightarrow \frac{V_1}{2} - \frac{V_1}{2} + \frac{V_2}{2} - \frac{V_1}{10} + \frac{V_3}{10} &= 0 \\
 \Rightarrow -\frac{11V_1}{10} + \frac{V_2}{2} + \frac{V_3}{10} &= 0 \dots \dots \dots (i)
 \end{aligned}$$

$$\begin{aligned}
 I_{R2} + I &= I_{R3} \\
 \Rightarrow \frac{V_1 - V_2}{R_2} + 3 &= \frac{V_2 - V_3}{R_3} \\
 \Rightarrow \frac{V_1}{2} - \frac{V_2}{2} + 3 - \frac{V_2}{2} + \frac{V_3}{2} &= 0 \\
 \Rightarrow \frac{V_1}{2} - V_2 + \frac{V_3}{2} &= -3 \dots \dots \dots (ii).
 \end{aligned}$$

$$\begin{aligned}
 I_{R3} + I_{R5} &= I_{R4} \\
 \Rightarrow \frac{V_2 - V_3}{R_3} + \frac{V_1 - V_3}{R_5} &= \frac{V_3 - 0}{R_4} \\
 \Rightarrow \frac{V_2}{2} - \frac{V_3}{2} + \frac{V_1}{10} - \frac{V_3}{10} - \frac{V_3}{4} &= 0 \\
 \Rightarrow \frac{V_1}{10} + \frac{V_2}{2} - \frac{17V_3}{20} &= 0 \dots \dots \dots (iii)
 \end{aligned}$$

From (i), (ii) and (iii),


$$-\frac{11V_1}{10} + \frac{V_2}{2} + \frac{V_3}{10} = 0$$

$$\frac{V_1}{2} - V_2 + \frac{V_3}{2} = -3$$

$$\frac{V_1}{10} + \frac{V_2}{2} - \frac{17V_3}{20} = 0.$$

$$\therefore V_1 = 3.68V, V_2 = 7.16V \text{ and } V_3 = 4.65V$$

(Ans)

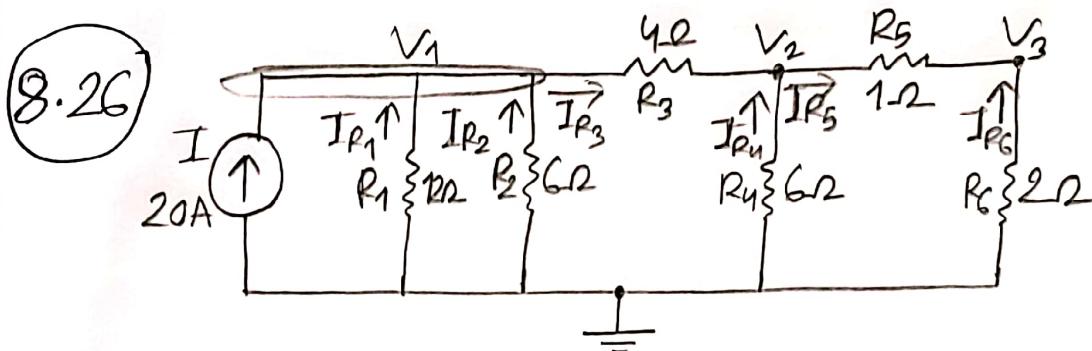

$$I + I_{R_1} + I_{R_2} = I_{R_3}$$

$$\Rightarrow 20 + \frac{0-V_1}{R_1} + \frac{0-V_1}{R_2} = \frac{V_1-V_2}{R_3}$$

$$\Rightarrow 20 + \frac{V_1}{12} - \frac{V_1}{6} = \frac{V_1}{4} - \frac{V_2}{4}$$

$$\Rightarrow \frac{V_1}{4} + \frac{V_1}{12} + \frac{V_1}{6} - \frac{V_2}{4} = 20$$

$$\Rightarrow \frac{V_1}{2} - \frac{V_2}{4} = 20 \dots \dots \dots \text{(i)}$$

$$I_{R_3} + I_{R_4} = I_{R_5}$$

$$\Rightarrow \frac{V_1-V_2}{R_3} + \frac{0-V_2}{R_4} = \frac{V_2-V_3}{R_5}$$

$$\Rightarrow \frac{V_1}{4} - \frac{V_2}{4} - \frac{V_2}{6} - \frac{V_2}{1} + \frac{V_3}{1} = 0$$

$$\Rightarrow \frac{V_1}{4} - \frac{17}{12} V_2 + V_3 = 0 \dots \dots \dots \text{(ii)}$$

$$I_{R_5} + I_{R_6} = 0.$$

$$\Rightarrow \frac{V_2 - V_3}{R_5} + \frac{0 - V_3}{R_6} = 0.$$

$$\Rightarrow \frac{V_2}{1} - \frac{V_3}{1} - \frac{V_3}{2} = 0.$$

$$\Rightarrow V_2 - \frac{3}{2}V_3 = 0 \dots \dots \text{(iii)}$$

From (i), (ii) and (iii),

$$\frac{V_1}{2} - \frac{V_2}{4} = 20$$


$$\frac{V_1}{4} - \frac{17}{12}V_2 + V_3 = 0$$

$$V_2 - \frac{3}{2}V_3 = 0.$$

$$\therefore V_1 = 48V, V_2 = 16V \text{ and } V_3 = 10.67V$$

(Ans)

8.27

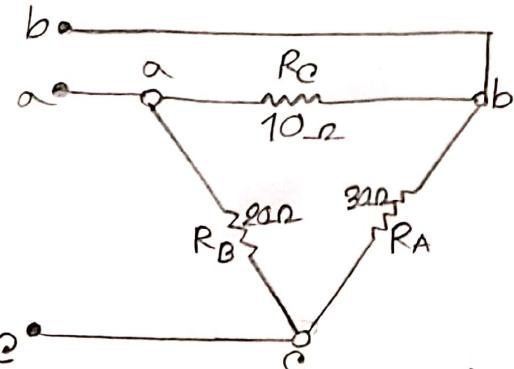


$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(20 \cdot 10)}{30 + 20 + 10} = \frac{200}{60} = 3.33\ \Omega$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(30 \cdot 10)}{30 + 20 + 10} = \frac{300}{60} = 5\ \Omega$$


$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(20 \cdot 30)}{30 + 20 + 10} = \frac{600}{60} = 10\ \Omega$$

(Ans)

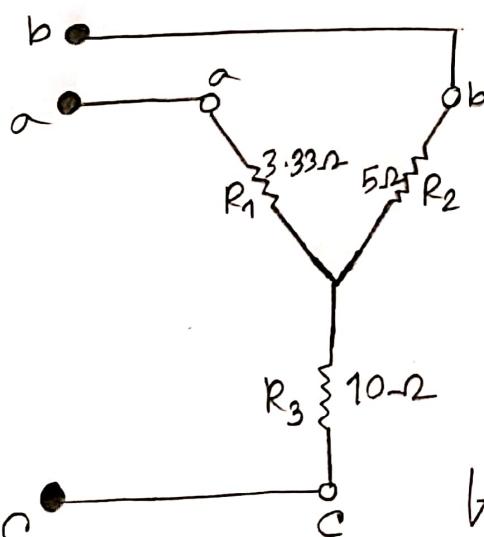

(Ans)

8.28

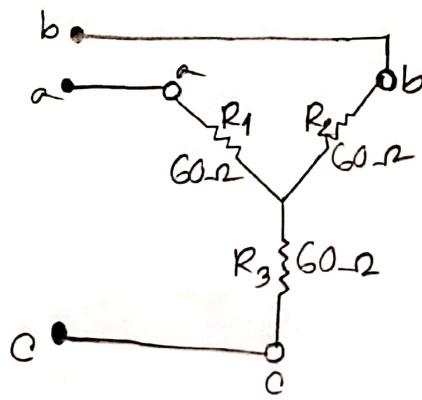

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} = \frac{(60, 60) + (60, 60) + (60, 60)}{60}$$


$$= \frac{3600 + 3600 + 3600}{60} = \frac{10800}{60} \Omega$$

$$= 180 \Omega$$

The three resistors for Δ are equal, so


$$R_A = 3R_\Delta = 3 \cdot (60 \Omega) = 180 \Omega$$
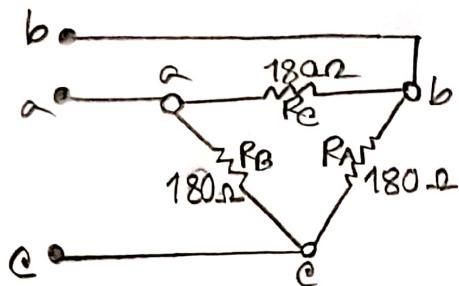
$$\therefore R_B = R_C = 180 \Omega \text{ (Ans)}$$



(Ans).


8.29

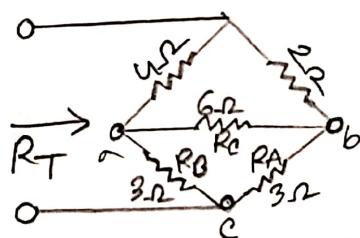

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3 \cdot 6)}{3 + 3 + 6} = \frac{18}{12} = 1.5 \Omega$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3 \cdot 6)}{3 + 3 + 6} = \frac{18}{12} = 1.5 \Omega$$
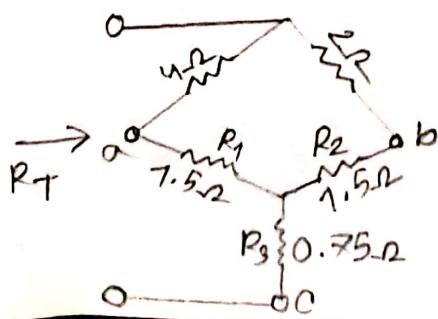
$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3 \cdot 3)}{3 + 3 + 6} = \frac{9}{12} = 0.75 \Omega$$




$$R_T = R_3 + \frac{(4+R_1)(2+R_2)}{(4+R_1)+(2+R_2)} = 0.75 + \frac{(4+1.5)(2+1.5)}{(4+1.5)+(2+1.5)}$$
$$= (0.75 + 2.139) \Omega$$


$$\therefore R_T = 2.89 \Omega \text{ (Ans)}$$

Chapter-09

9.1

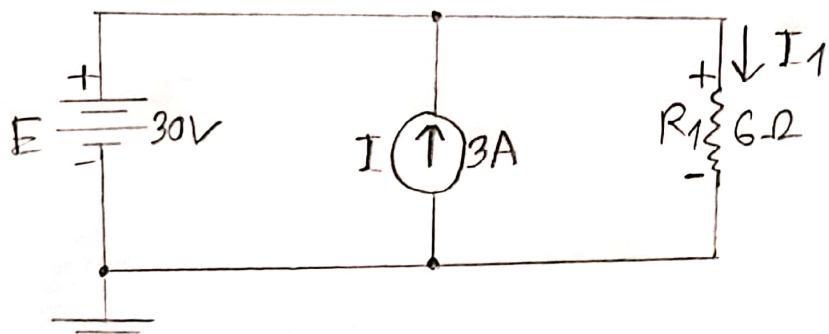


Determining the effect of the $E=30V$,

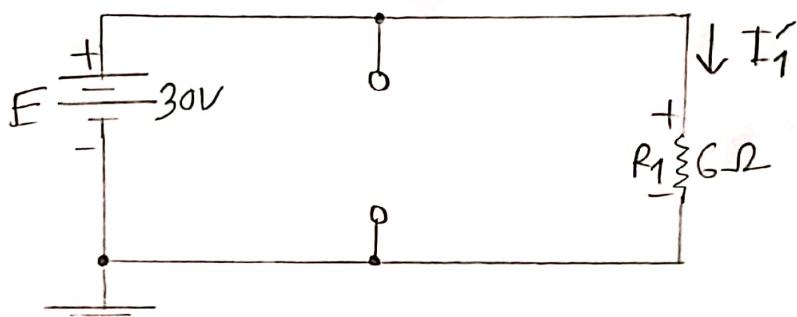

$$\therefore I_1' = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{30V}{6\Omega} = 5A \downarrow$$

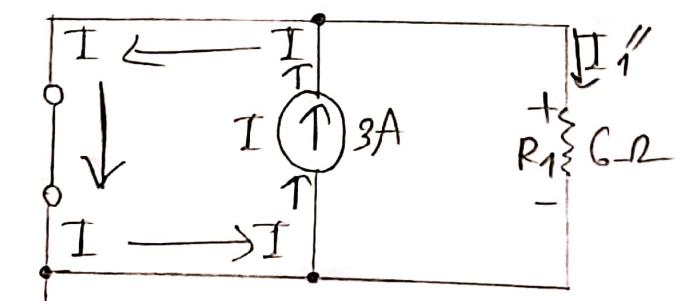Determining the effect of the 3A current source,




$$\therefore I_1'' = \frac{R_{sc} I}{R_{sc} + R_1} = \frac{0 \cdot 3}{0 + 6} = 0A$$


$$\therefore I_1 = I_1' + I_1'' = 5A + 0A = 5A \downarrow$$

(Ans)

9.2

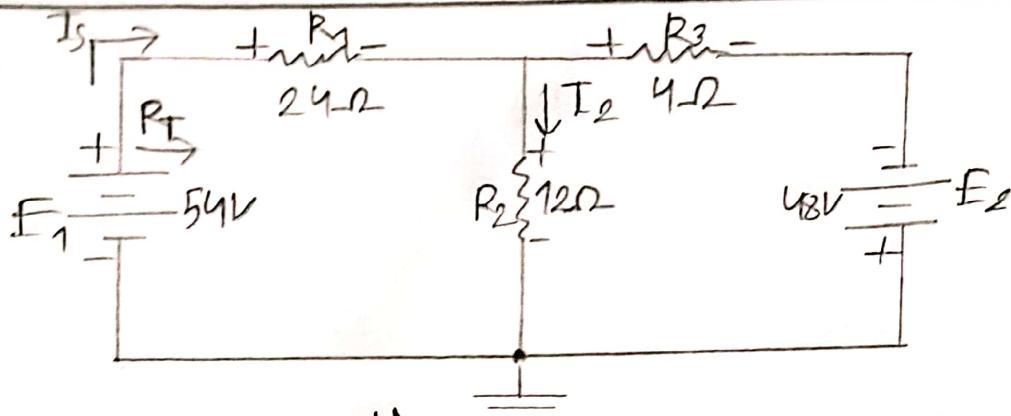

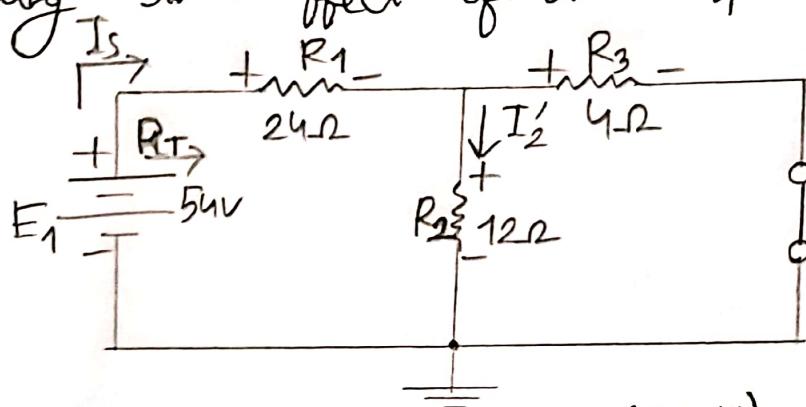Determining the effect of the $E_1 = 54V$,




$$\text{Hence, } R_T = R_1 + \frac{R_2 R_3}{R_2 + R_3} = \left(24 + \frac{(12 \cdot 4)}{12+4} \right) \Omega = 27 \Omega$$

$$I_S = \frac{E_1}{R_T} = \frac{54V}{27\Omega} = 2A.$$

$$\therefore I_2' = \frac{R_3 I_S}{R_3 + R_2} = \frac{(4 \cdot 2)}{4+12} = 0.5A \downarrow$$

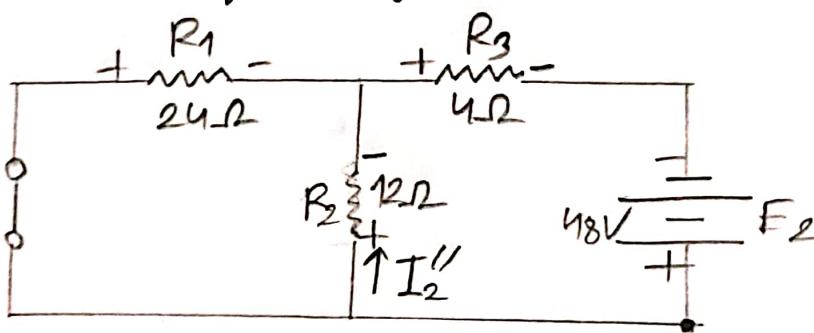Determining the effect of the $E_2 = 48V$,




$$\text{Hence, } R_T = R_3 + \frac{R_2 R_1}{R_2 + R_1} = \left(4 + \frac{(12 \cdot 24)}{12+24} \right) \Omega = 12 \Omega$$

$$\therefore I_S = \frac{E_2}{R_T} = \frac{48V}{12\Omega} = 4A$$


$$\therefore I_2'' = \frac{R_1 I_S}{R_1 + R_2} = \frac{(24 \cdot 4)}{24+12} = 2.67A \uparrow$$

$$\therefore I_2 = I_2'' - I_2' = (2.67 - 0.5)A = 2.17A \uparrow \\ (\text{Ans})$$

(9.3)

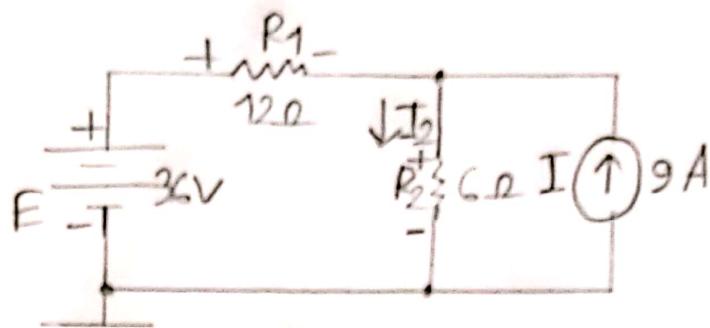


Determining the effect of the $E = 36V$,

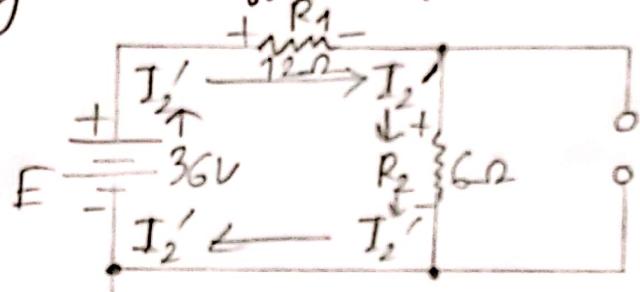

$$\therefore I_2' = \frac{E}{R_T} = \frac{E}{R_1 + R_2} = \frac{36}{12 + 6} A = 2A \downarrow$$

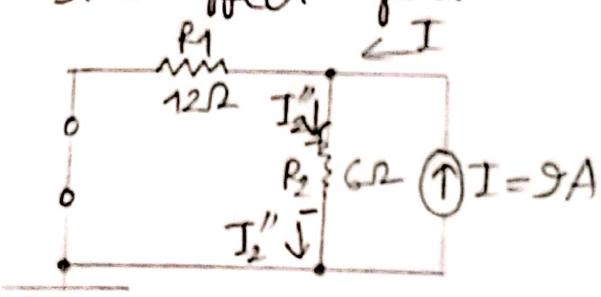Determining the effect of the 9A current source,



$$\therefore I_2'' = \frac{R \cdot I}{R_1 + R_2} = \frac{(12 \cdot 9)}{12 + 6} A = 6A \downarrow$$

$$\therefore I_2 = I_2' + I_2'' = (2 + 6)A = 8A \downarrow \\ (\text{Ans})$$


$$\therefore P_1 = (I_2')^2 (R_2) = (2)^2 \cdot 6 = 24W$$

$$\therefore P_2 = (I_2'')^2 (R_2) = (6)^2 \cdot 6 = 216W$$

$$\therefore P_T = I_2^2 R_2 = (8)^2 \cdot 6 = 384W$$


$$\therefore P_1 + P_2 = (24 + 216)W = 240W \neq P_T = 348W.$$

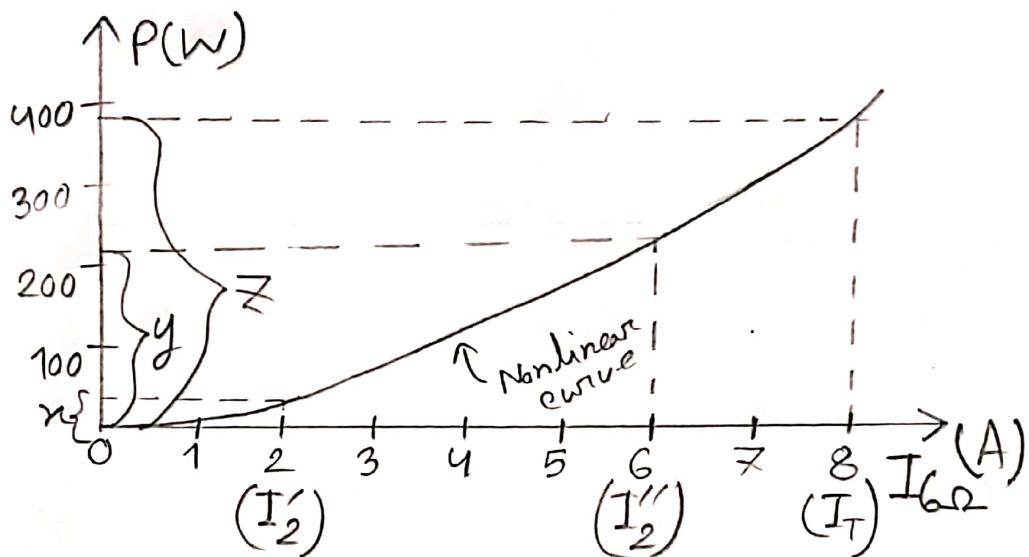Therefore, the superposition theorem is not applicable to power levels. (Ans).



plotting power delivered to the 6Ω resistor versus current through transistors

Here, $a+b \neq z$

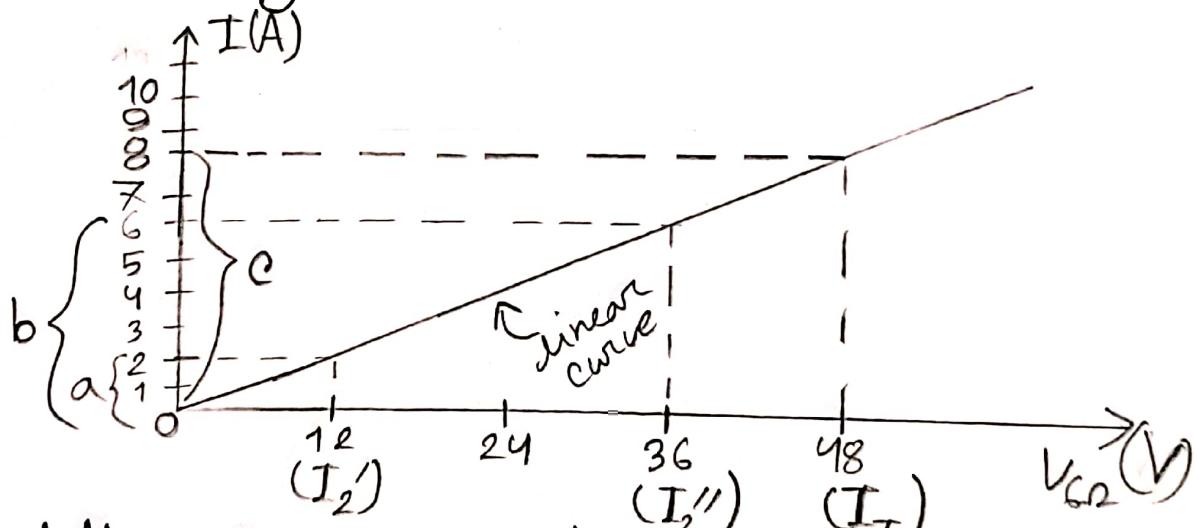


plotting I versus V for the 6Ω resistor


Here,

$$c = a+b. \quad (\text{Ans})$$


9.4

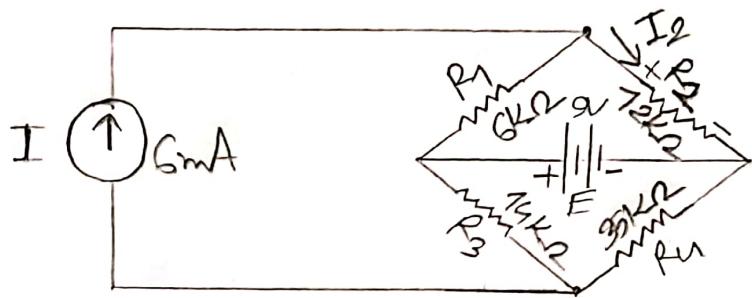

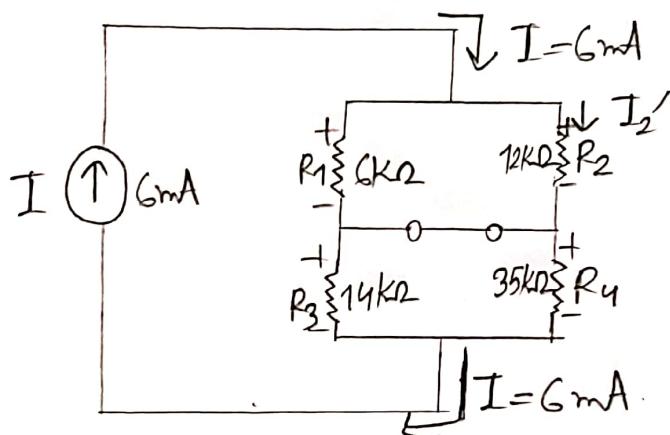Determining the effect of the 6mA current source,


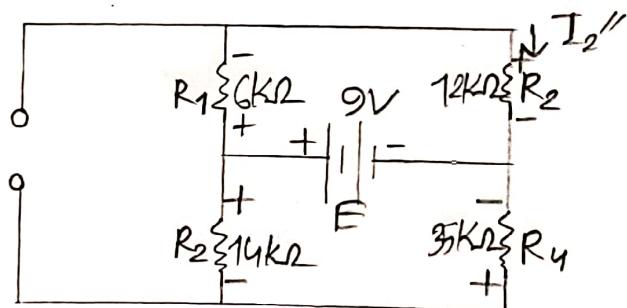
$$\therefore I_2' = \frac{R_1 I}{R_1 + R_2} = \frac{(6 \cdot 6)}{6 + 12} = 2\text{mA} \downarrow$$




$$\therefore I_2'' = \frac{E}{R_1 + R_2} = \frac{9}{6 + 12} \text{mA} = 0.5\text{mA} \downarrow$$


$$\therefore I_2 = I_2' + I_2'' = 2\text{mA} + 0.5\text{mA} = 2.5\text{mA} \downarrow$$

(Ans)

9.5

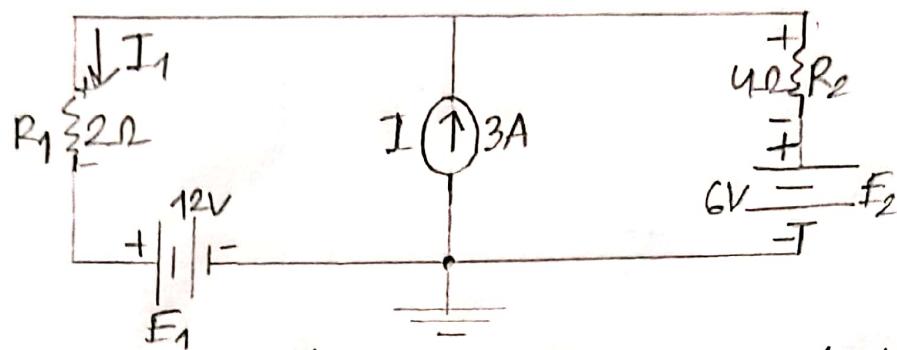


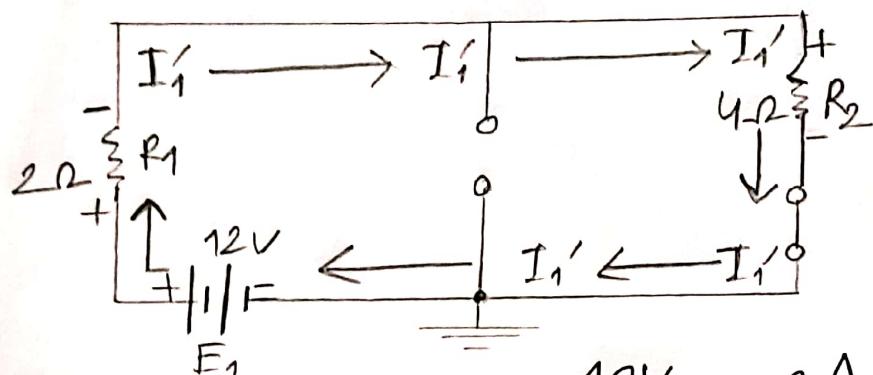Determining the effect of the $E_1 = 12V$,




$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12V}{2\Omega + 4\Omega} = \frac{12V}{6\Omega} = 2A \uparrow$$

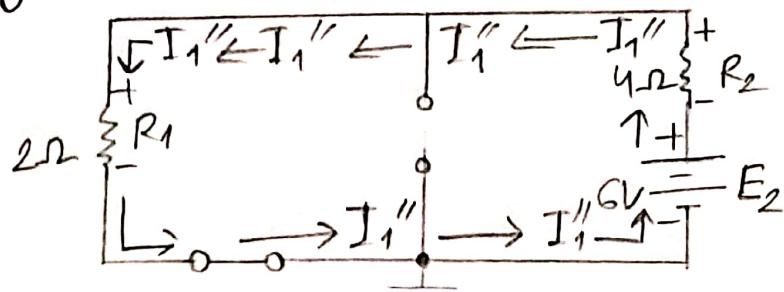Determining the effect of the $E_2 = 6V$,



$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6V}{2\Omega + 4\Omega} = \frac{6V}{6\Omega} = 1A \downarrow$$

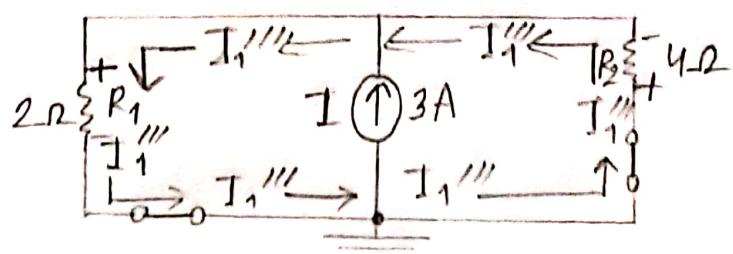Determining the effect of the 3A current source,




$$I_1'' = \frac{R_2 I}{R_1 + R_2} = \frac{(4 \cdot 3)}{2+4} A = 2A \downarrow$$


$$\therefore I_1 = -I_1' + I_1'' + I_1''' = -2A + 1A + 2A = 1A \downarrow$$

(Ans).

Q.6

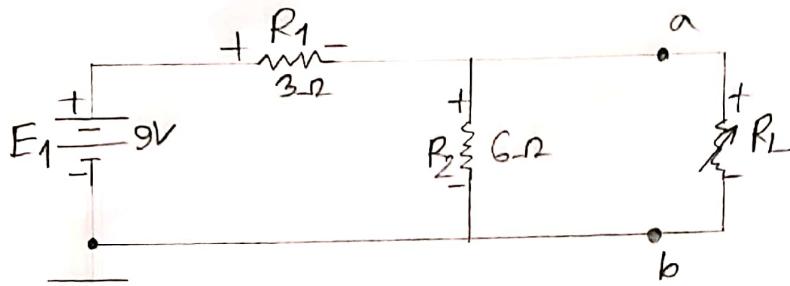


Determining R_{Th} ,

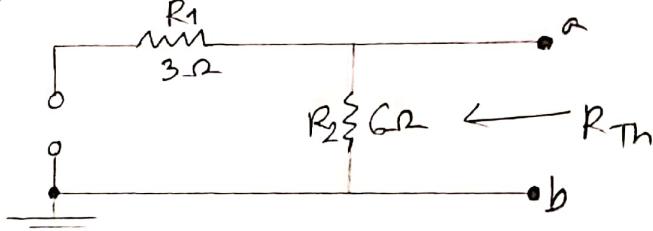

$$R_{Th} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{(3 \cdot 6)}{3+6} \Omega = 2\Omega$$

$$\therefore R_L = R_{Th} = 2\Omega$$

Determining E_{Th} ,

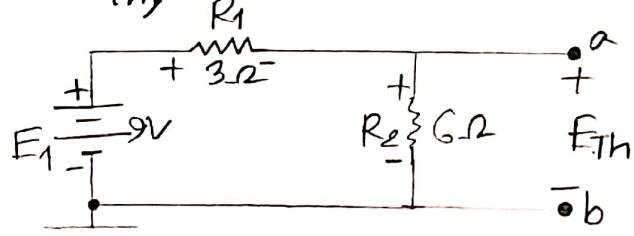

$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{(6 \cdot 9)}{6+3} V = 6V$$

$$\text{we know, } I_L = \frac{E_{Th}}{R_{Th} + R_L}$$


$$\therefore R_L = 2\Omega ; I_L = \frac{R_{Th} + R_L}{6V} = 1.5A$$

$$\therefore R_L = 10\Omega ; I_L = \frac{6V}{2\Omega + 10\Omega} = 0.5A$$


$$\therefore R_L = 100\Omega ; I_L = \frac{6V}{2\Omega + 100\Omega} = 0.06A$$

(Ans)

9.7

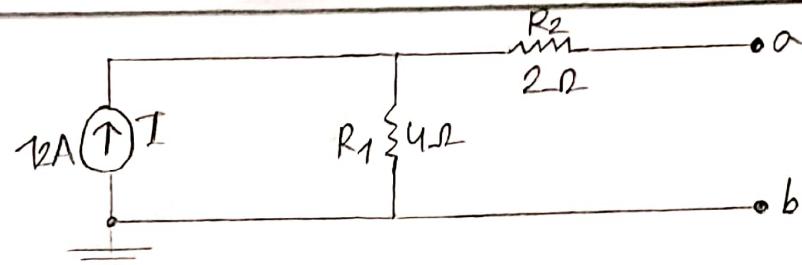


Determining R_{Th} ,

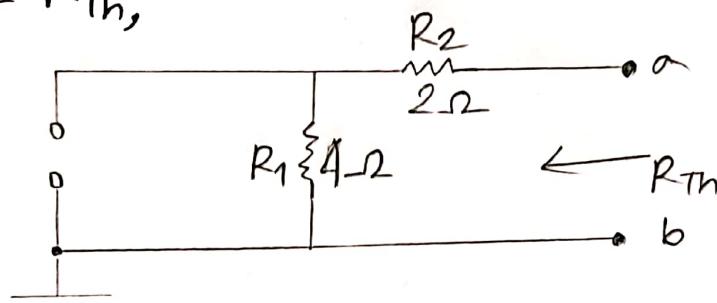


$$R_{Th} = R_1 + R_2 = (4\Omega + 2\Omega) = 6\Omega$$

Determining E_{Th} ,

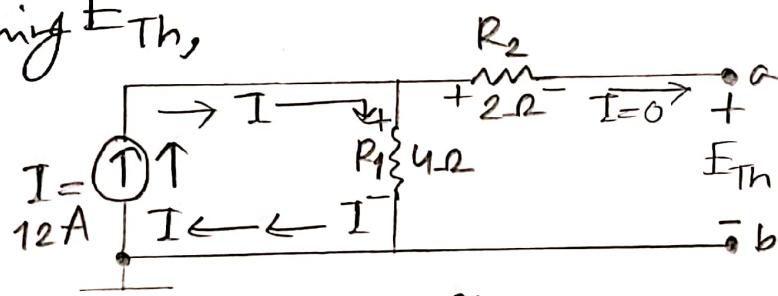



$$\text{Here, } V_2 = I_2 R_2 = (0.2)V = 0V$$
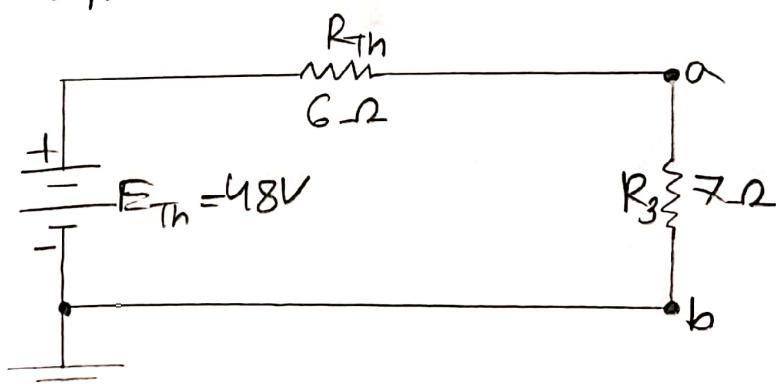
$$\therefore E_{Th} = V_1 = I_1 R_1 = (12 \cdot 4)V = 48V$$




(Ans)


9.8

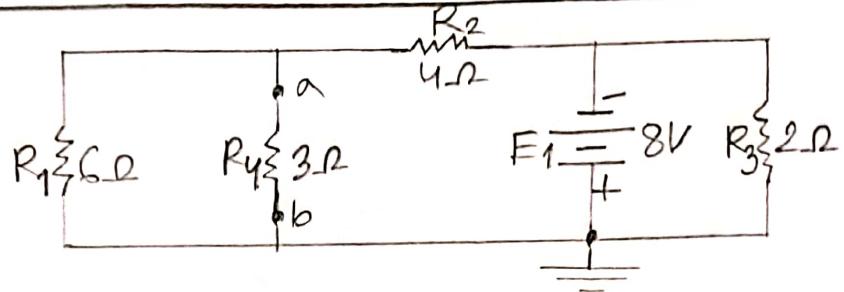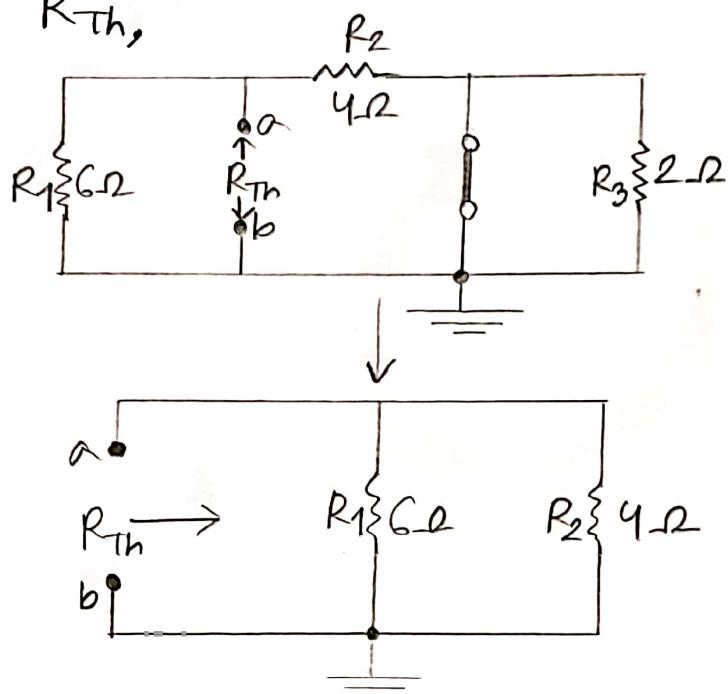Determining R_{Th} ,


$$R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{(6 \cdot 4)}{6+4} \Omega = 2.4 \Omega$$

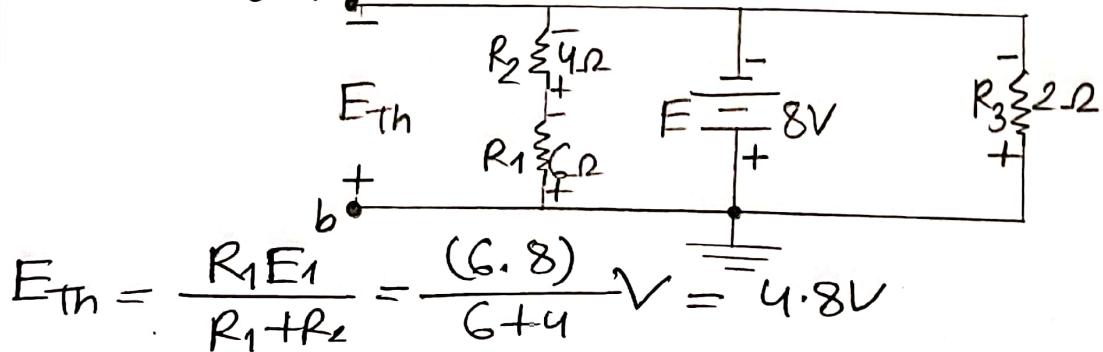Determining E_{Th} ,

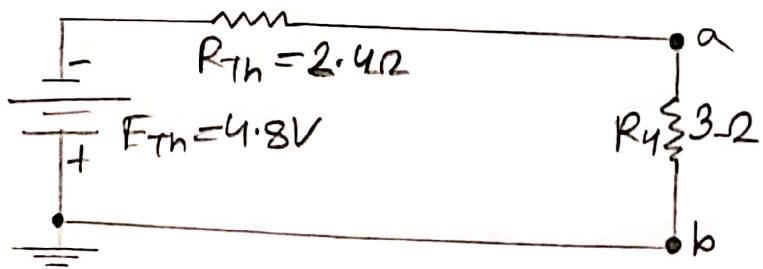
$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \cdot 8)}{6+4} V = 4.8V$$



9.10

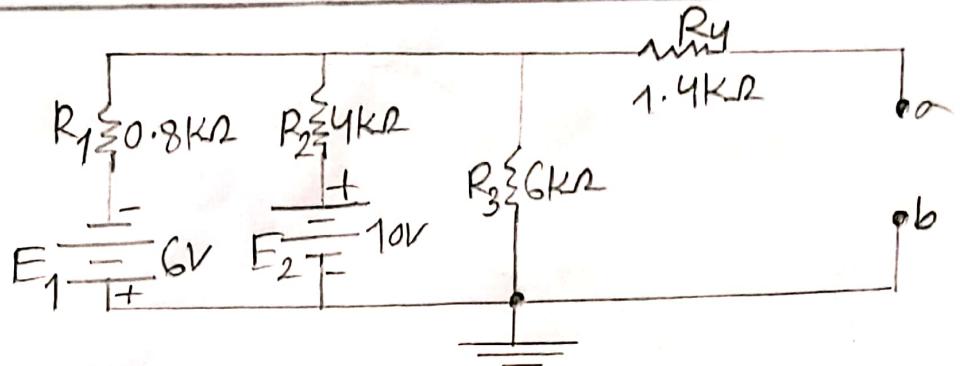


Determining R_{Th} ,

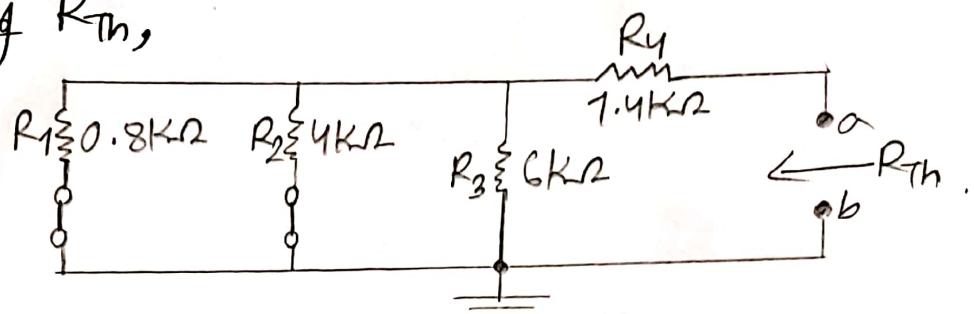

$$\begin{aligned}
 R_{Th} &= R_y + R_1 \parallel R_2 \parallel R_3 \\
 &= R_y + R_1 \parallel \frac{R_2 R_3}{R_2 + R_3} \\
 &= R_y + R_1 \parallel \frac{(4 \cdot 6)}{4 + 6} \\
 &= R_y + R_1 \parallel 2.4 \\
 &= R_y + \frac{(0.8 \cdot 2.4)}{0.8 + 2.4} \\
 &= 1.4 + 0.6 \\
 &= 2 \text{ k}\Omega
 \end{aligned}$$

Determining E'_{Th} ,

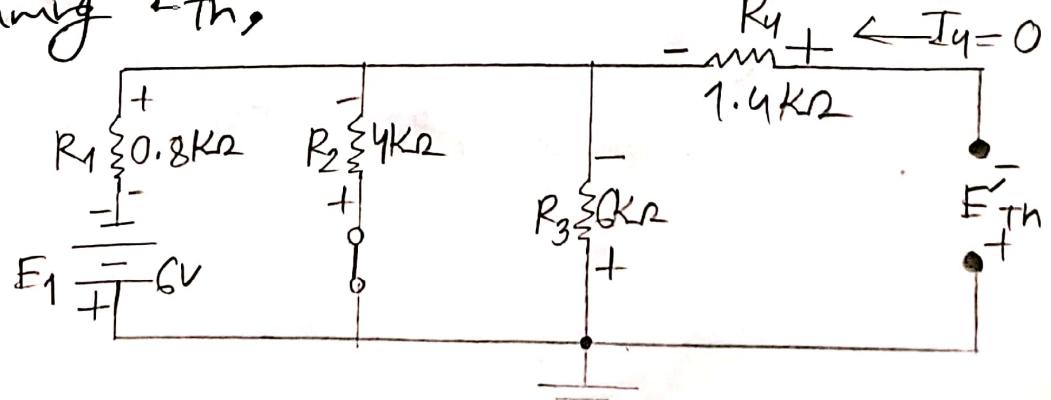


$$E'_{Th} = V_3$$

$$R_T' = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{(4 \cdot 6)}{4+6} \Omega = 2.4 \text{ k}\Omega$$

$$V_3 = \frac{R_T' E_1}{R_T' + R_1} = \frac{(24.6)}{2.4 + 0.8} V = 4.5 V = E_{Th}'$$

Determining E_{Th}'' ,

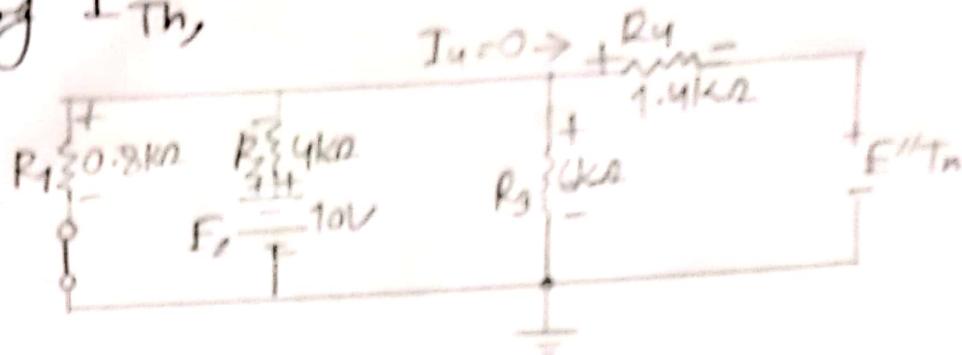


$$E_{Th}'' = V_3$$

$$R_T' = R_1 \parallel R_3 = \frac{R_1 R_3}{R_1 + R_3} = \frac{(0.8 \cdot 6)}{0.8 + 6} \Omega = 0.706 \text{ k}\Omega$$

$$V_3 = \frac{R_T' \cdot E_1}{R_T' + R_2} = \frac{(0.706 \cdot 10)}{0.706 + 4} V = 1.5 V = E_{Th}''$$



Since E_{Th}' and E_{Th}'' have opposite polarities,
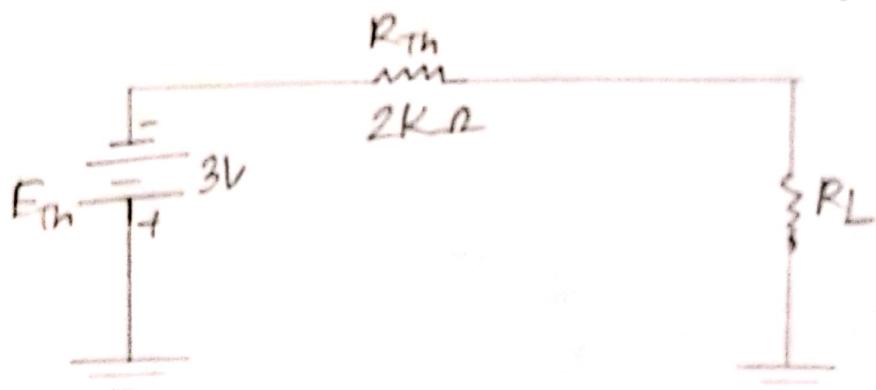
$$E_{Th} = E_{Th}' - E_{Th}'' = (4.5 V - 1.5 V) = 3 V \quad (\text{polarity of } E_{Th})$$




(A_m).


9.11

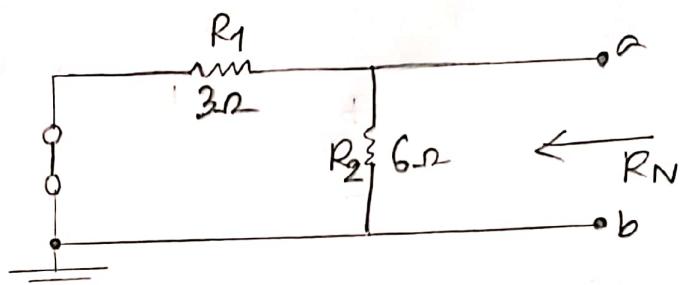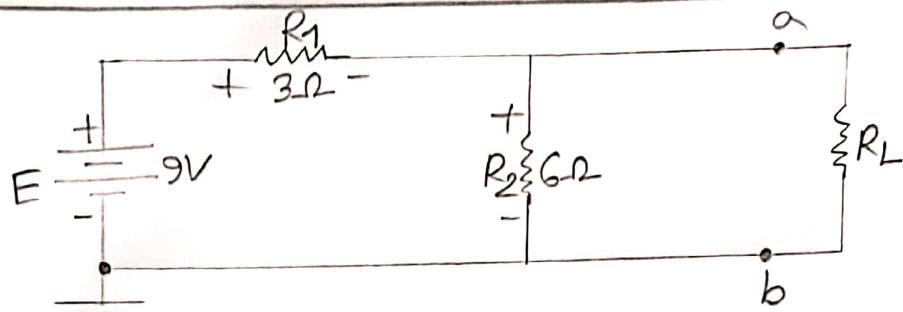
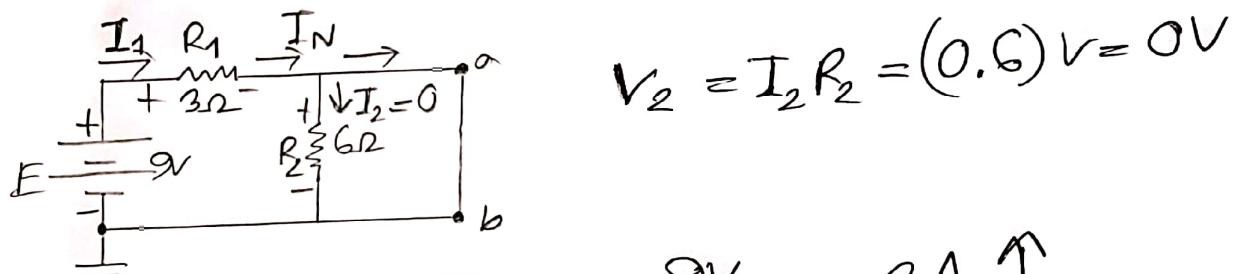
$$R_N = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{3 \cdot 6}{3 + 6} = 2\Omega$$


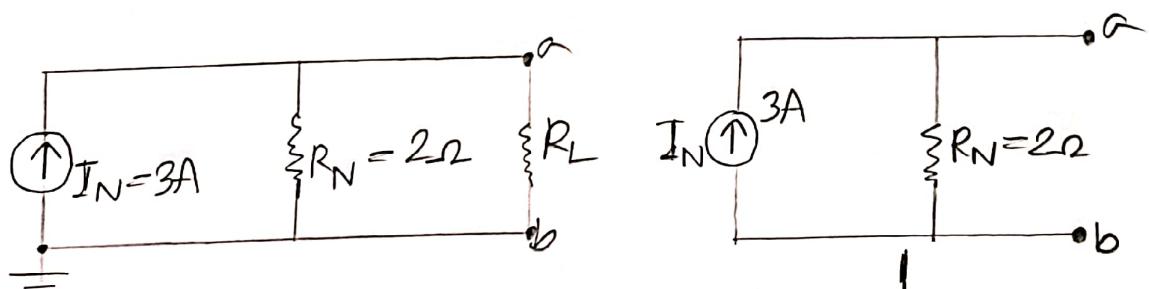
$$\text{Therefore, } I_N = \frac{E}{R_N} = \frac{9V}{2\Omega} = 3A \uparrow$$





$$R_{Th} = R_N = 2\Omega$$


$$E_{Th} = I_N R_N = (3A \cdot 2\Omega) = 6V$$

(Ans)


Q. 12

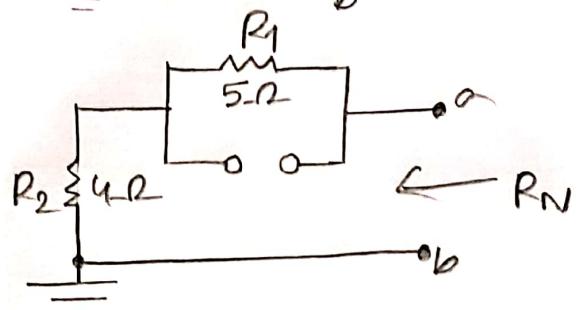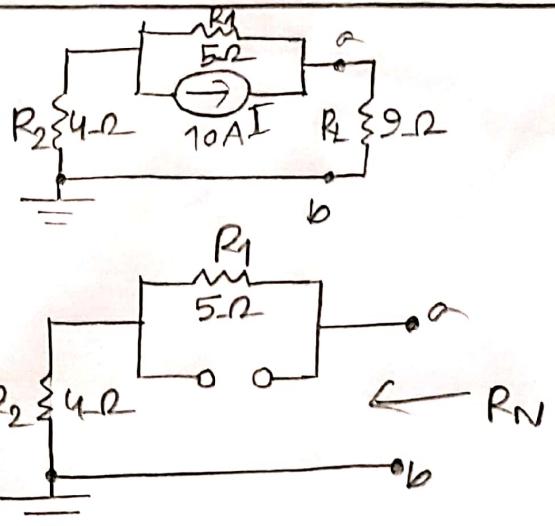
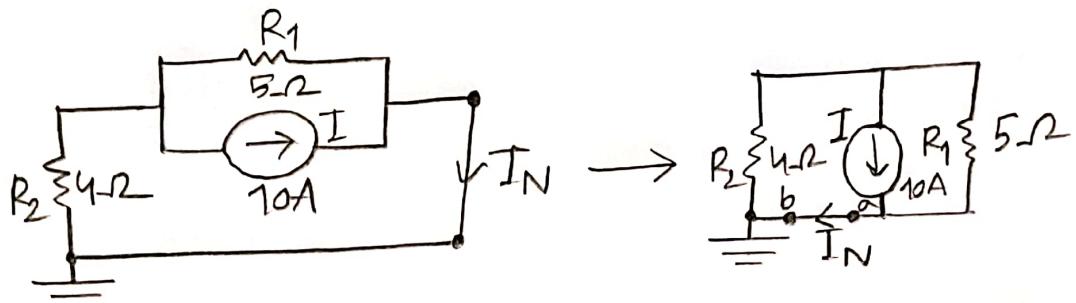
$$R_N = R_1 + R_2 = (5 + 4)\Omega = 9\Omega$$




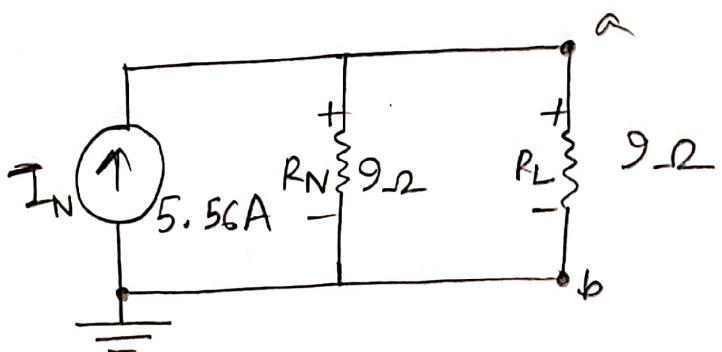
$$I_N = \frac{R_1 I}{R_1 + R_2} = \frac{(5 \cdot 10)}{5 + 4} = 5.56A \uparrow$$




(Ans).


9.13

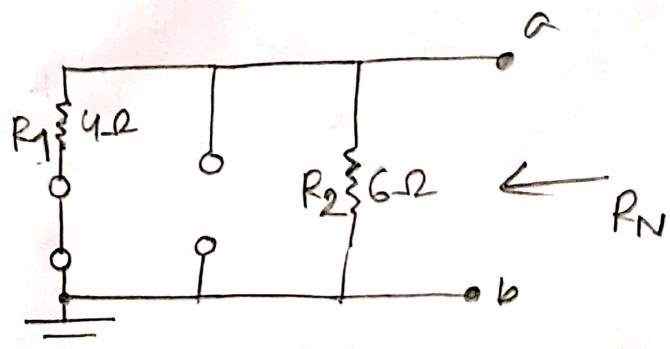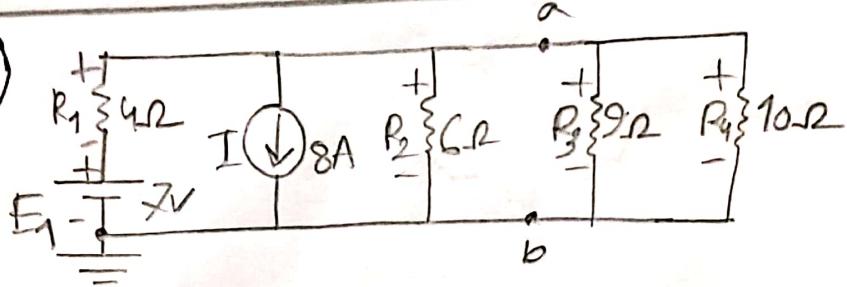
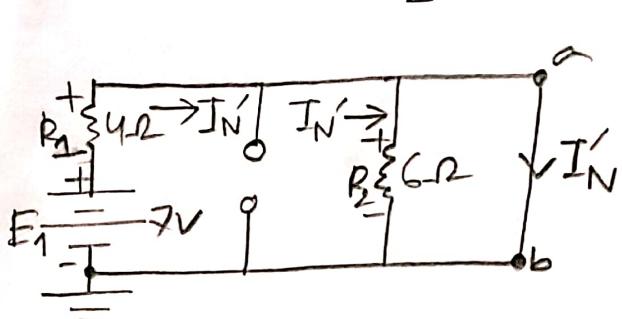
$$R_N = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{(4 \cdot 6)}{4+6} = 2.4\Omega$$



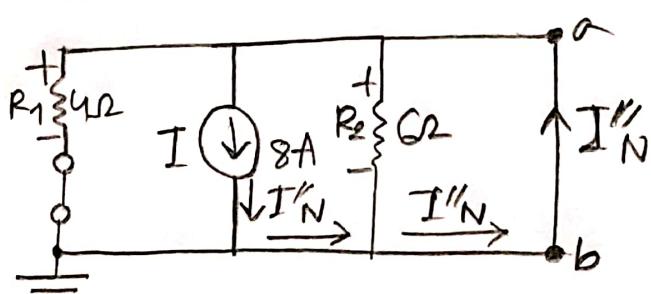
$$I_{N'} = \frac{E_1}{R_1} = \frac{7V}{4\Omega} = 1.75A \downarrow$$




$$I_{N''} = I = 8A \uparrow$$
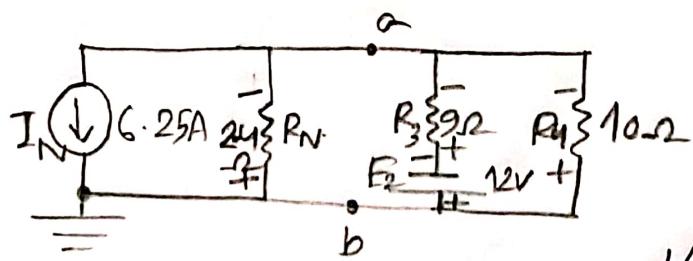
$$\therefore I_N = I_{N''} - I_{N'} = 8A - 1.75A = 6.25A \uparrow$$




(Ans)

9.17

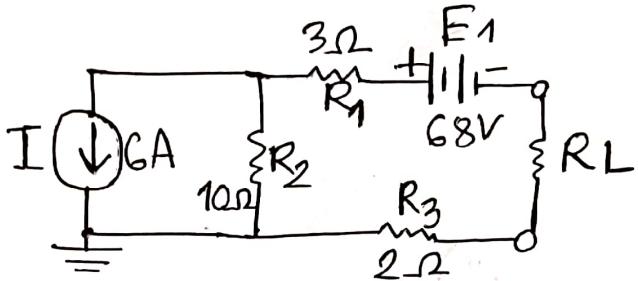


Determining R_{Th} ,

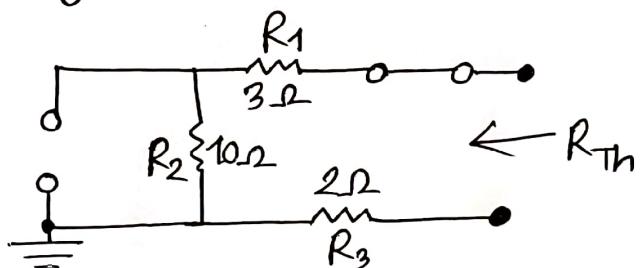

$$R_{Th} = R_1 + R_2 + R_3 = (3 + 10 + 2) \Omega = 15 \Omega \text{ (Ans)}$$

$$\therefore R_L = R_{Th} = 15 \Omega$$

Determining E_{Th} , $V_1 = 0$

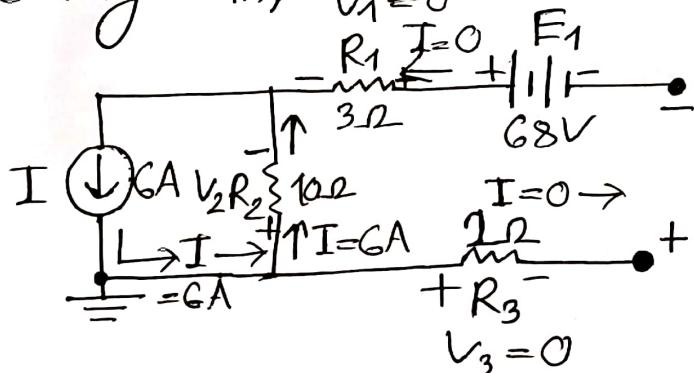

$$\text{Here, } V_1 = V_3 = 0 \text{ and } V_2 = I_2 R_2 = IR_2 = (6 \cdot 10) V = 60 V$$

So,

$$-V_2 - E + E_{th} = 0$$

$$\Rightarrow E_{th} = 60 V + 68 V = 128 V \text{ (Ans)}$$

$$\therefore E_{th} = 128 V$$

$$\therefore P_{Lmax} = \frac{E_{th}^2}{4R_{Th}} = \frac{(128)^2}{4 \cdot 15} W = 273.07 W \text{ (Ans)}$$